

FIRST SEMESTER

B.Tech. (GROUP-A)

MID SEMESTER EXAMINATION

SEPTEMBER 2014

EE-105 ELECTRICAL SCIENCES

Time: 1 Hour 30 Min

Max. Marks: 20

Note: Answer any five questions. All questions carry equal marks.
Assume the missing data suitably (if any)

1. Find the Thevenin's equivalent circuit of the network shown in Fig. 1. [4]

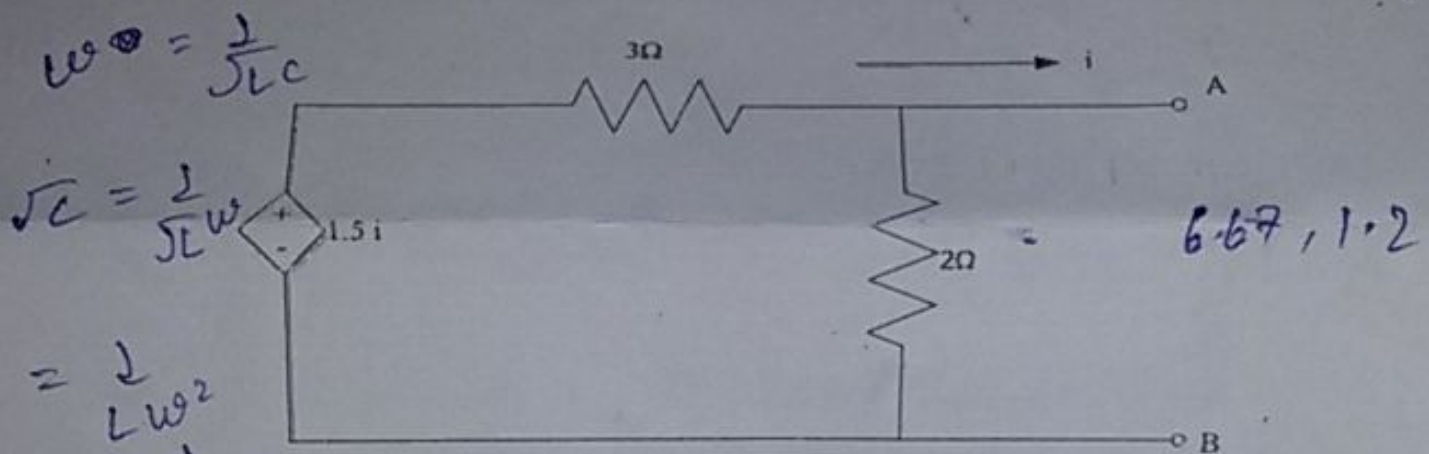


Fig. 1.

2. Find the value of capacitance (C) so that resonance occurs in the circuit shown in Fig. 2. [4]

$$1.014 \times 10^{-3}$$

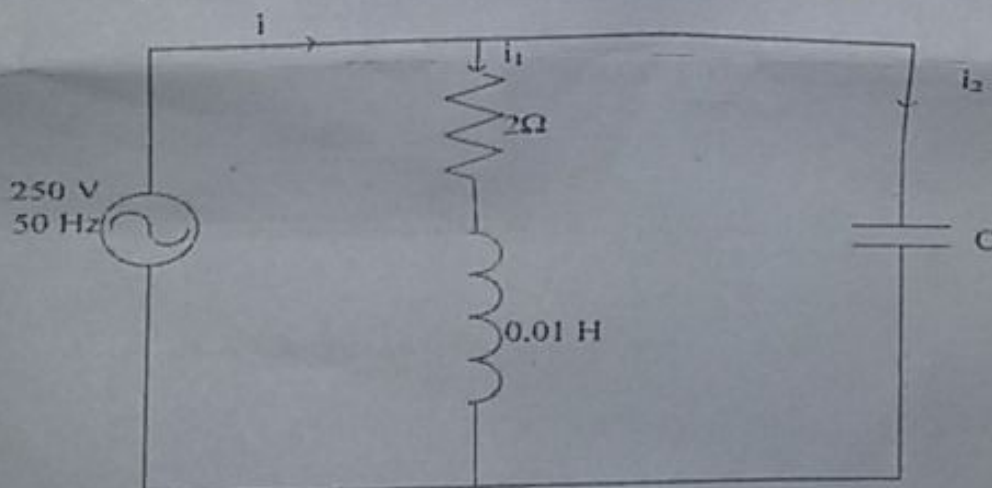


Fig. 2

3. Draw the approximate phasor diagram for the circuit shown in Fig. 3. [4]

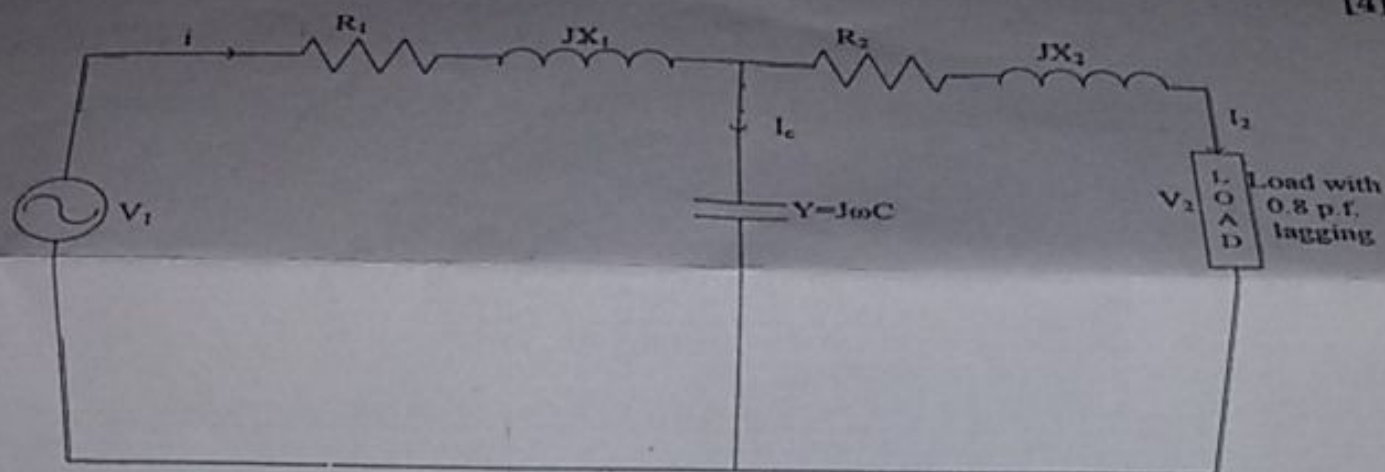


Fig. 3

4. What is the potential difference between X and Y of the network shown in Fig. 4. [4]

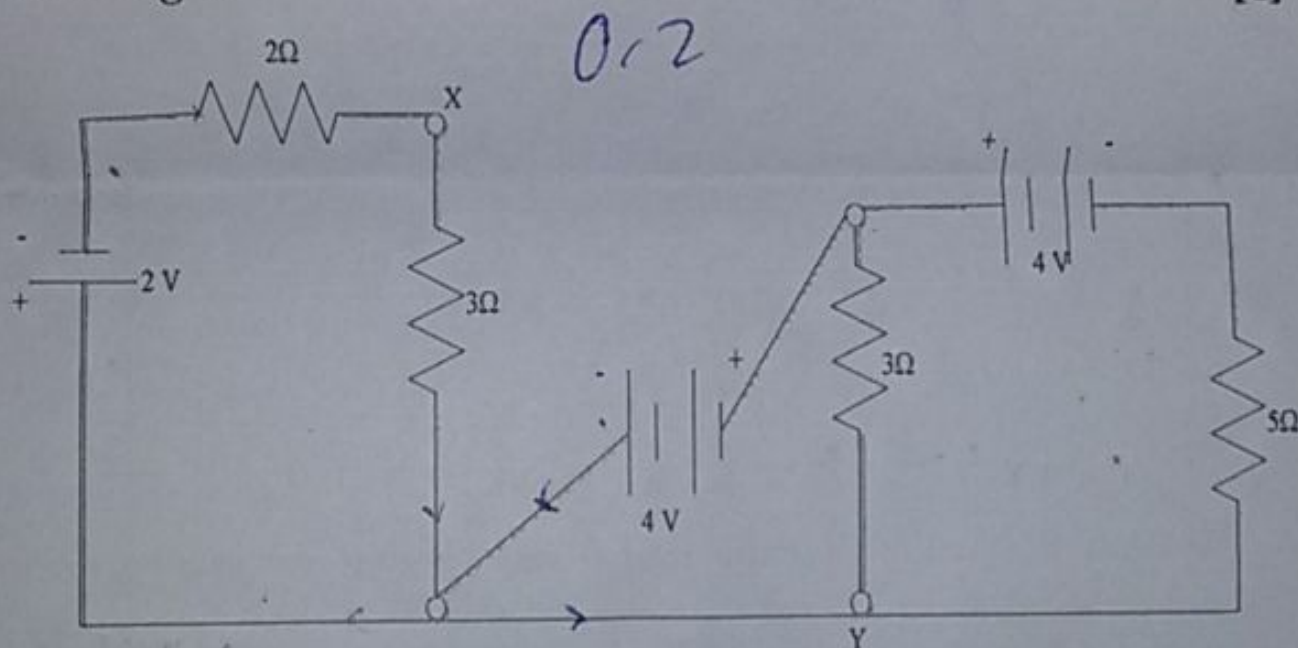


Fig. 4

5. Define the following terms: [4]
 (a) Quality factor (b) Form factor (c) Bandwidth (d) Resonance
6. State and explain superposition theorem with the help of suitable example. [4]
