
A . C C I R C U I T S

UNIT ~~II~~ II


E L E C T R I C A L S C I E N C E

Prof. N. K. Jain.

First Year First Year First Semester



Some Definitions

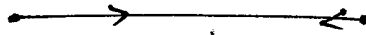direction of Current $\frac{1}{\text{ }}$



Unidirectional Current

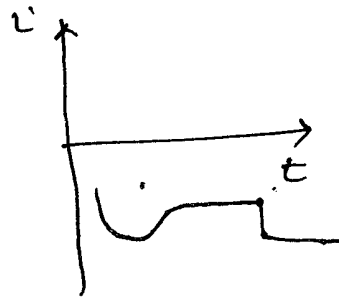
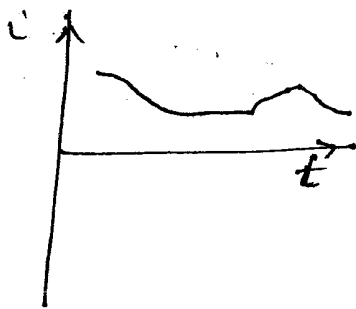
If the average current flow over a specified period of time through a conductor always remains ~~one~~ in one direction only, it is called unidirectional current



(A)

Direct Current (D.C.)

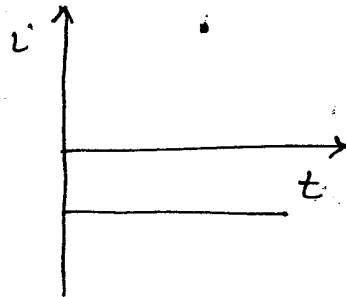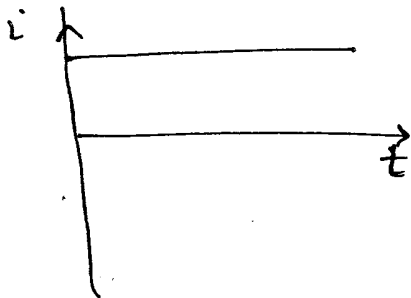If the magnitude of the current remains constant, it is called Direct Current (D.C.)




(B)

Pulsating Current

It is a ~~direct or~~ unidirectional current with current magnitude varies with time. Fig (A).

Alternating Current

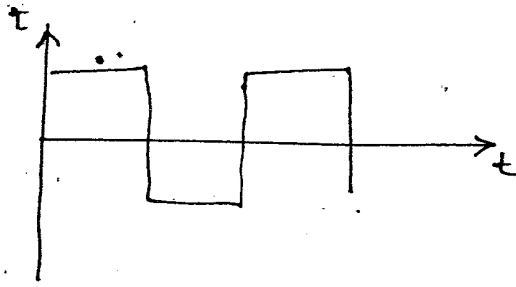
A current which keeps on changing its direction continually is called an alternating current. The +ve and -ve parts are similar.




(C)

Periodic Current

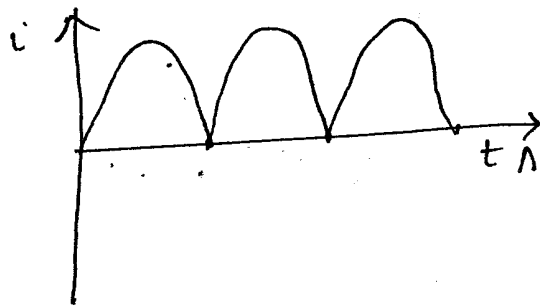
If the ~~magnitude~~ magnitude and direction of the current varies periodically, it is called periodic current



periodic unidirectional
direct current

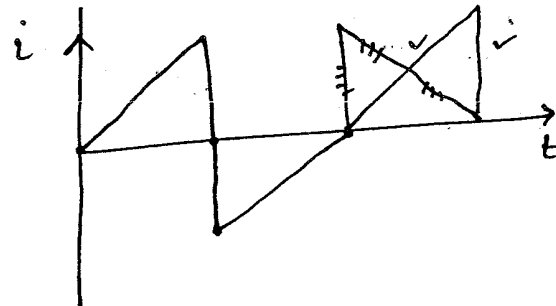

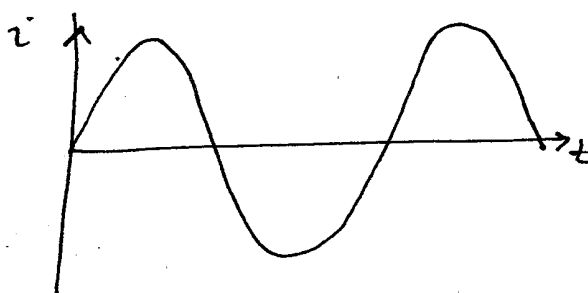Periodic Alternating
Current (Triangular)



— di —
(Sinusoidal)

Pulsating Current

If the +ve and -ve halves of an alternating current are not similar, it said to be pulsating current



Maximum Power Transfer Theorem

OT
(3)

Therefore,

For D.C.

1. D.C. flows in one direction i.e. it doesn't change its sign with time.
2. Any D.C. source has 2 terminals. One is marked +ve and the other as -ve. Conventional current flows from +ve terminal to the -ve terminal of the source (for outside the source).

For A.C

1. A.C. changes its magnitude and sign periodically.
2. The wave shape of A.C. may have any shape, but for electrical supply sinusoidal wave form is used.

The Advantages of Sinusoidal Waveform

1. Many phenomena occurring in nature are of sinusoidal nature e.g. simple pendulum and guitar string.
2. The sinusoidal function has an interesting characteristic mathematical.
 - Its integral and derivatives are both sinusoids.
 - So in a linear circuit the response to a sinusoid forcing function would also be sinusoid. This makes the mathematical analysis

- 4
3. The application of sinusoidal voltage to appropriately designed coils results in a revolving magnetic field which has capacity to do work.

The majority of electric motors work on this principle.

4. - The knowledge of the response of electric circuits to sinusoidal functions has mathematical advantage. ~~the~~
- We know that any periodic function can be represented in terms of an infinite series of sinusoids using Fourier series
 - This means, response of an electric circuit to a non-sinusoidal forcing function can be obtained through a repeated application of the sinusoidal theory.
5. • When a sinusoidal voltage across a coil, the current also remains sinusoidal.
• For other waveforms it is not true.
6. - If input to a transformer is sinusoidal, output also remains sinusoidal
- This means the sinusoidal voltage generated by an Electric Supply Company reaches the Consumer

- 58
7. AC generators has comparatively lesser cost than DC generators for the same rating.
 8. Much higher voltages can be generated in AC as compared to DC
 9. Use of transformers is possible only in AC
 10. AC motors are cheaper than DC motors in initial cost as well as in maintenance
 11. Switchgears for AC are simpler than that required for a DC system.
 12. However, DC transmission has its own advantages. That is why HVDC transmission is being adopted now a days.

Generation of Alternating EMF

Story of Faraday and Cavendish.


According to Faraday's laws an emf is induced (generated) whenever there is a relative motion ~~in the mag~~ between the magnetic field and the conductor.


This can be ~~made~~ manipulated in two ways.

1. rotating a coil in a stationary magnetic field
 2. Rotating a magnetic field with in a station coil.
- ① is adopted for small ac generators
 - ② " " " large " "

The magnitude of the emf generated depends upon

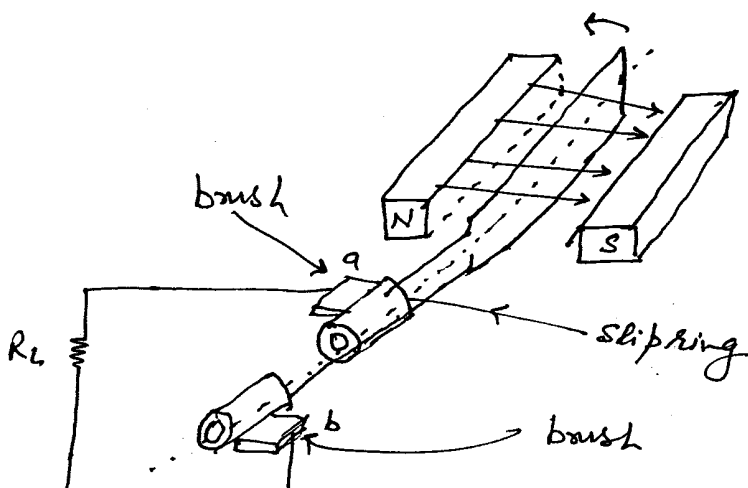1. the number of turns on the coil (N)
2. the strength of magnetic field (Φ_m)
3. the speed at which the coil/magnetic field rotates (ω) radians/sec



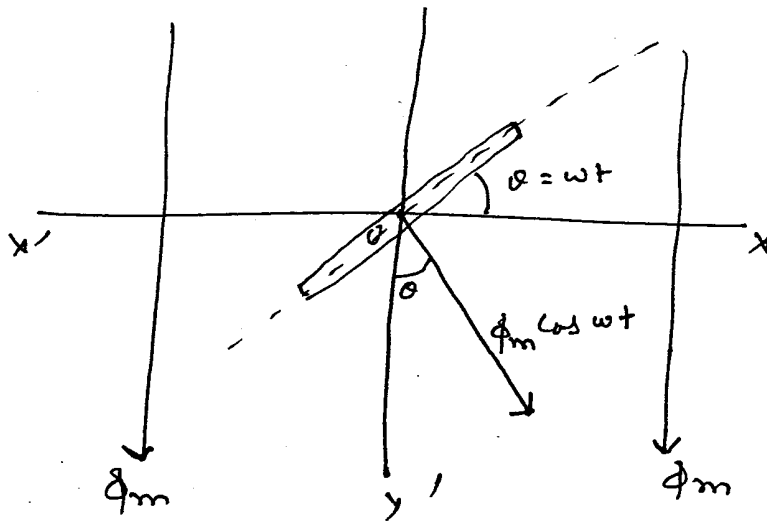

- Let the time be measured from the instant of coincidence of the plane of the coil with x-axis
- At this instant the maximum flux ϕ_m links with the coil.
- Let us consider an instant after a time of t seconds as shown in figure.

$$\theta = \omega t$$

Component of flux along \perp to the plane of coil

$$= \phi_m \cos \omega t$$

Flux linkages at this instant


$$= N \cdot \phi_m \cos \omega t$$

$$\text{emf induced } e = -\frac{d}{dt} [N \phi_m \cos \omega t]$$

$$= \phi_m N \frac{d}{dt} [-\cos \omega t] = \phi_m N \omega \sin \omega t \quad \text{--- (1)}$$

$$= E_m \sin \omega t$$

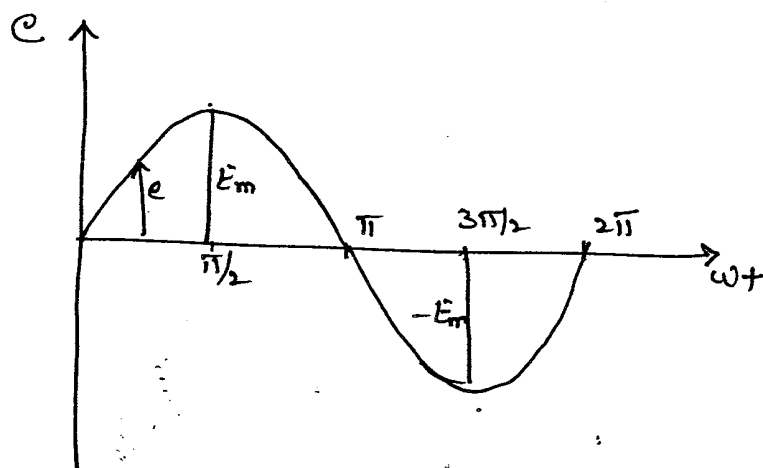Therefore, the following waveform can be drawn.



e = instantaneous value of emf $wt=0$

E_m = Maximum value of emf $wt = \pi/2 + 3\pi/2$

ω = angular velocity in radians/sec.

f = frequency in cycles/sec.

in each rotation the radians covered = 2π

$$\therefore \omega = 2\pi f$$

$$\therefore e = E_m \sin \omega t = E_m \sin 2\pi f t$$

Average Value

Arithmetically we define average value as

$$= \frac{\text{Sum of all values}}{\text{no. of values.}}$$

But in case of a waveform, we would like to define the average value as.

$$\frac{\text{the area under the waveform}}{\text{Length of one cycle.}}$$

The area under +ve half cycle (Fig. A) is equal to the area under -ve half cycle in magnitude, but opposite in sign, so, strictly speaking the total

For this reason, we will talk for the average value over the half cycle.

For full cycle

$$E_{av} = \frac{1}{2\pi} \int_0^{2\pi} e \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} e \, d(\omega t)$$
$$= \frac{1}{T} \int_0^T v \cdot dt = 0 \text{ for full cycle.}$$

~~For half~~

$$= \frac{1}{2\pi} \int_0^{2\pi} E_m \sin \theta \, d\theta = \frac{E_m}{2\pi} \left[-\cos \theta \right]_0^{2\pi}$$
$$= -\frac{E_m}{2\pi} \left[-1 - (-1) \right] = 0$$

For half cycle


$$E_{av} = \frac{1}{\pi} \int_0^{\pi} e \, d\theta = \frac{1}{\pi} \int_0^{\pi} E_m \sin \theta \, d\theta$$
$$= \frac{E_m}{\pi} \int_0^{\pi} \sin \theta \, d\theta = \frac{E_m}{\pi} \left[-\cos \theta \right]_0^{\pi}$$
$$= \frac{E_m}{\pi} \left[-(-1) - (-1) \right] = \frac{E_m}{\pi} [1+1] = \frac{2E_m}{\pi}$$

$E_{av} = 0.637 E_m$


Similar expression can be derived for current.

PRO

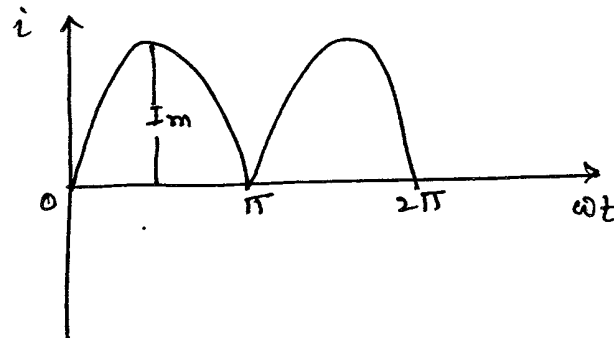Work down average values of the following waves by inspection. 10




$$I_{av} = 0.637 I_m$$

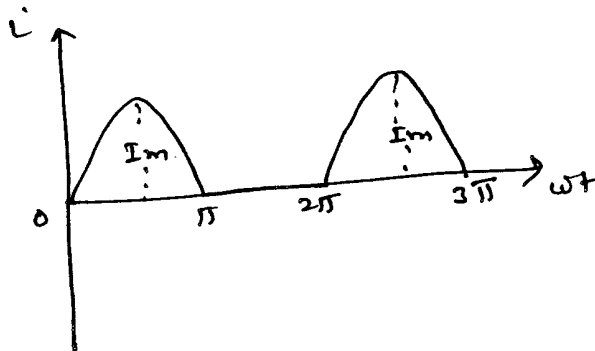

$$I_{av} = 0.318 I_m$$

Effective Value


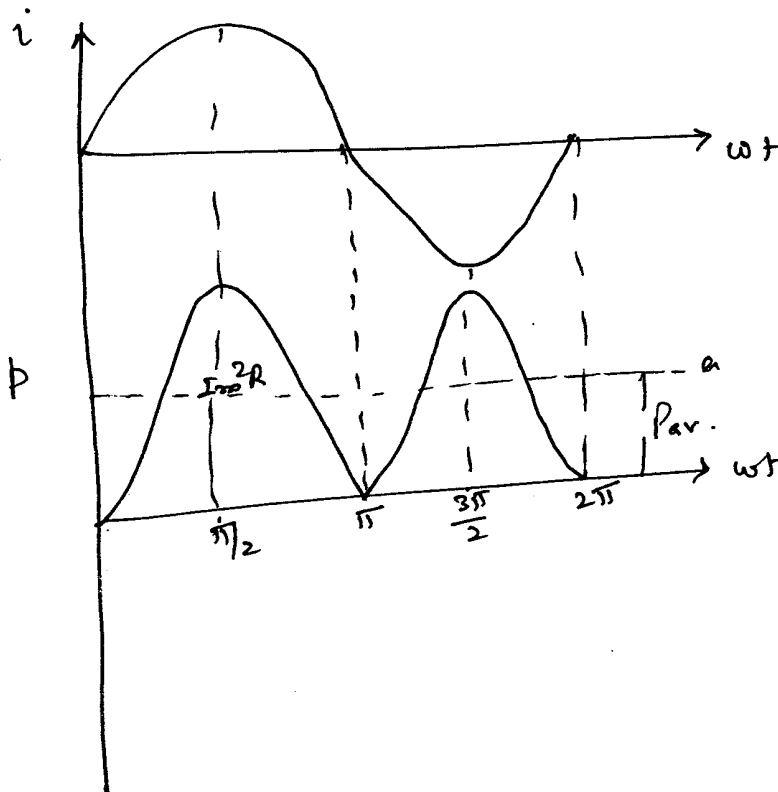


(A)

(B)

The effective value of an ac current is defined as that value of a direct current which when allowed to through a given circuit for a given time produces the equal amount of heat as produced by the ac current when allowed to flow through the same circuit for the same time.

consider

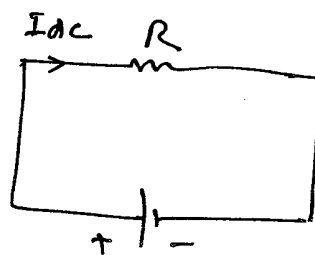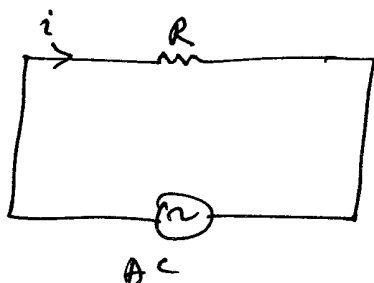

$$i = I_m \sin \omega t$$

$$p = i^2 R \quad \text{waveform for } p \text{ is shown fig (B).}$$

The average value of p over a complete cycle be represented by P_{av} .

- We are interested to find I_{dc} which gives power equal to P_{av} .

$$i = I_m \sin \omega t$$

$$p = i^2 R = R I_m^2 \sin^2 \omega t$$

$$= \frac{R I_m^2}{2} (1 - \cos 2\omega t) = \frac{R I_m^2}{2} - \frac{R I_m^2}{2} \cos 2\omega t$$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} p \, d\omega t = \frac{1}{2\pi} \int_0^{2\pi} \left[\underbrace{\frac{R I_m^2}{2}}_{\text{constant}} - \underbrace{\frac{R I_m^2}{2} \cos 2\omega t}_{\int=0} \right] d\omega t$$

- The I term is constant & independent of ωt
- I of II term ...

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} \frac{R I_m^2}{2} \cdot d\omega t - \frac{1}{2\pi} \int_0^{2\pi} \frac{R I_m^2}{2} \cos 2\omega t (d\omega t). \quad 12$$

$$= \frac{1}{2\pi} \left[\frac{R I_m^2}{2} \right] \omega t \Big|_0^{2\pi} - \frac{1}{2\pi} \cdot \frac{R I_m^2}{2} \left[\frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{1}{2\pi} \left[\frac{R I_m^2}{2} \right] [2\pi - 0] - \frac{1}{2\pi} \cdot \frac{R I_m^2}{2} \left[\frac{\sin 4\pi - \sin 0}{2} \right]$$

$$= \frac{R I_m^2}{2}$$

For d.c.

$$P_{dc} = I_{dc}^2 R = P_{av} = \frac{R I_m^2}{2}$$

$$I_{dc}^2 = \frac{I_m^2}{2}$$

$$I_{dc} = \sqrt{\frac{I_m^2}{2}} = \frac{1}{\sqrt{2}} I_m = 0.707 I_m = I_{eff} = I_{rms}$$

I_{rms} = root mean square

Justification of rms

$$p = i^2 R$$

$$P_{av} = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T i^2 R dt$$

$$= \left[\frac{1}{T} \int_0^T i^2 dt \right] \cdot R = I_{eff}^2 R$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

root
mean
square

rms value > Average value except for rectangular wave for which

rms value = Average value.

- V and I without any subscript means rms values
- V_{rms} , V_{eff} are not necessary ~~an~~ except, where a confusion may exist.
- Any specification made without any reference means rms value.

Form Factor

$$= \frac{\text{effective value}}{\text{average value}}$$

$$= \frac{V_{rms}}{V_{av}} = \frac{0.707 V_m}{0.637 V_m} = 1.11$$

Peak Factor

$$= \frac{V_{max}}{V_{rms}} = \frac{V_m}{V_m / \sqrt{2}} = \sqrt{2} = 1.414$$

Example 1, Find the rms value of a resultant current in a wire, which carries simultaneously a direct current of 5A, and a sinusoidal a.c. with a peak value of 5A.

Soln: - Let I be the rms value of the resultant current.

- rms value is defined on the basis of energy consumption

$$\begin{aligned}\therefore I^2 R_t &= I^2 R_t + \left(\frac{5}{\sqrt{2}}\right)^2 R_t \\ &= \left[5^2 + \left(\frac{5}{\sqrt{2}}\right)^2\right] R_t\end{aligned}$$

$$I^2 = 5^2 + \left(\frac{5}{\sqrt{2}}\right)^2 = 25 + 12.5 = 37.5$$

$$I = \sqrt{37.5} = \underline{6.12 \text{ A}}$$

Alternatively,

by definition of rms value

$$\begin{aligned}I &= \sqrt{\frac{5^2 + \left(\frac{5}{\sqrt{2}}\right)^2}{1}} = \sqrt{25 + 12.5} = \sqrt{37.5} \\ &= \underline{6.12 \text{ A}}\end{aligned}$$

Example 2: Calculate the rms value of current given by $i = 10 + 5 \cos(628t + 30^\circ)$

$$\begin{aligned}I_{\text{rms}} &= \sqrt{10^2 + \left(\frac{5}{\sqrt{2}}\right)^2} = \sqrt{100 + 12.5} \\ &= \sqrt{112.5} = \underline{10.61 \text{ A}}\end{aligned}$$

Example 3: Compute the maximum and rms values of the following quantities

(i) $40 \sin \omega t$ (ii) $(A+B) \sin(\omega t - \pi)$

(iii) $10 \sin \omega t - 17.3 \cos \omega t$.

Soln: (i)

$$I_m = 40$$

$$I_{\text{rms}} = \frac{40}{\sqrt{2}} = \underline{28.28}$$

(ii)

$$I_m = \underline{A+B}$$

$$I_{\text{rms}} = \underline{\underline{\frac{A+B}{\sqrt{2}}}}$$


(iii)

P.T.O

Phasor Diagrams

Rotating Bar

Explain step by step

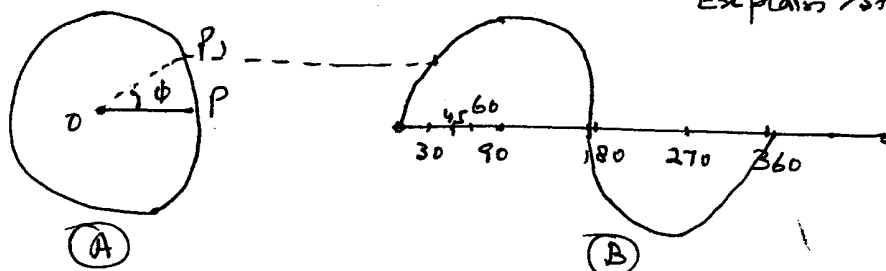


OP is phasor representation, OP gives max value.

$$v = V_m \sin \omega t$$

OP rotates at angular velocity of ω radians/sec.

Fig. (A) and (B) give the same information.

Consider 2 phasors

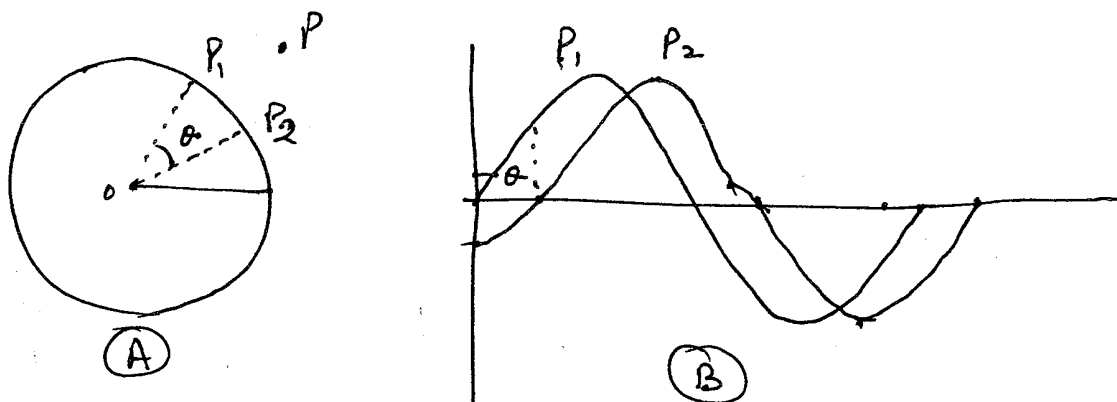

P_2 lags P_1 by θ i.e.

$$\text{if } v_1 = V_m \sin \omega t$$

$$v_2 = V_m \sin(\omega t - \theta)$$

- If we do our work only with Fig (A), it would be complete.
- We normally represent electrical data in terms of rms values.
- Nothing will be lost if OP, represents rms value in place of max. value.

Such representation is called phasor representation.

- Phasor representation in form (A) is of a little meaning, if only one phasor.
- Phasor representation would serve better purpose if more than one phasor are involved.
- Phasor diagrams represents the relative positions of phasors at an instant of time
- Phasors are rotating vectors.
- rms values are taken on phasor diagrams
- For drawing phasor diagrams we need to take a reference phasor.
- It is to be selected conveniently
- For series circuits current is taken as reference phasor for convenience
- For parallel circuits voltage is taken as reference phasor for convenience.

Algebraic Operations on Phasors

- These are done similar to vectors which you have studied in your school.

- There are two forms in which phasors are represented

• Polar Form : $A \angle \theta$

• Rectangular Form : $x + jy$ $j = \sqrt{-1}$

$$\left. \begin{aligned} A &= \sqrt{x^2 + y^2} & \theta &= \tan^{-1}\left(\frac{y}{x}\right) \\ x &= A \cos \theta & y &= A \sin \theta \end{aligned} \right\} \textcircled{A}$$

Addition and Subtraction of Phasor

- For this the phasors should be represented in rectangular form

$$A \angle \theta_1 + B \angle \theta_2$$

$$(A \cos \theta_1 + j A \sin \theta_1) + (B \cos \theta_2 + j B \sin \theta_2)$$

$$= (A \cos \theta_1 + B \cos \theta_2) + j (A \sin \theta_1 + B \sin \theta_2)$$

Multiplication of Phasors

- For this phasors should be represented in polar form

$$A \angle \theta_1 \times B \angle \theta_2 = A \cdot B \angle \theta_1 + \theta_2$$

$$\frac{A \angle \theta_1}{B \angle \theta_2} = \left(\frac{A}{B}\right) \angle \theta_1 - \theta_2$$

- Change of phasors from polar form to rectangular form and vice versa is to be done frequently. This can be done using (A) In calculations

22

Example 1: Determine the phase difference of the phasor $i_1 = 40 \sin(100\pi t + 30^\circ)$ wrt.

$i_2 = 60 \sin(100\pi t)$ in terms of time and draw the phasor diagram to represent the two phasors.


Soln: $\omega = 2\pi f = 100\pi$ $f = 50 \text{ Hz}$

$$T = \frac{1}{f} = \frac{1}{50} \text{ sec.}$$

The full revolution (360°) for either phasor is $(1/50)$ sec. The time taken to cover 30° is

$$t = \frac{1}{50} \cdot \frac{30}{360} = \frac{1}{600} \text{ sec} = \underline{1.67 \text{ ms}}$$

Phasor i_1 leads i_2 by 30° . So phasor diagram is:

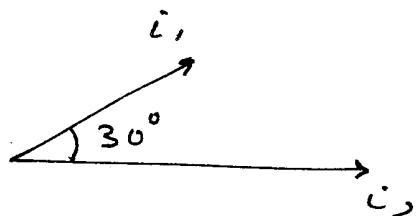

Example 2: A current $I = 4 + j3$ amperes is flowing through a resistor of 10Ω . How much power is being consumed by the resistor?

Soln: $I = 4 + j3 = \sqrt{4^2 + 3^2} \tan^{-1} 3/4$
 $= 5 \angle 36.87^\circ$

$$P = I^2 R = 5^2 \cdot 10 = \underline{250 \text{ W}}$$

The power due to real component of current

$$P_1 = 4^2 \cdot 10 = 16 \cdot 10 = 160 \text{ W}$$

Power due to imaginary component of current

$$P_2 = 3^2 \cdot 10 = 9 \cdot 10 = 90 \text{ W.}$$

2.

Conclusion: The imaginary part of the current also carries real power.

Comment: 1. The concept of complex numbers i.e. real numbers and imaginary numbers is a mathematical concept and doesn't mean that imaginary numbers are for ~~imaginal~~ imagination only. They don't have any real implication.

BUT

imaginary numbers are as real as real numbers.

2. Your imaginations/belief has real effect ~~on~~ in your life.

Example 3: Determine $10 \angle 0^\circ + 20 \angle 60^\circ$

Soln: $I_1 = 10 \angle 0^\circ = 10 + j0$

$$I_2 = 20 \angle 60^\circ = 20 \cos 60^\circ + j 20 \sin 60^\circ \\ = 10 + j 10 \sqrt{3}$$

$$I_1 + I_2 = (10 + 10) + j 10 \sqrt{3} = 20 + j 10 \sqrt{3} \\ = \underline{26.46 \angle 40.9^\circ}$$

Example 4: Determine $I = I_1 + I_2 + I_3$

$$i_1 = 5 \sin \omega t \quad i_2 = 5 \sin (\omega t + 30^\circ)$$

$$i_3 = 5 \sin (\omega t - 120^\circ)$$

Soln:

$$I_1 = \frac{5}{\sqrt{2}} \angle 0 = \frac{5}{\sqrt{2}} + j0 = 3.536 + j0$$

$$I_2 = \frac{5}{\sqrt{2}} \angle 30^\circ = \frac{5}{\sqrt{2}} \cos 30 + j \frac{5}{\sqrt{2}} \sin 30$$

$$= 3.06 + j 1.768$$

$$I_3 = \frac{5}{\sqrt{2}} \angle -120^\circ = \frac{5}{\sqrt{2}} (\cos(-120^\circ) - j \sin(-120^\circ))$$

$$= -1.768 - j 3.06$$

$$I = I_1 + I_2 + I_3 = (3.536 + 3.06 - 1.768) + j$$
$$+ j (1.768 - 3.06)$$

$$= 4.828 - j 1.292 = 5 \angle \tan^{-1} \frac{-1.292}{4.828}$$

$$= \underline{5 \angle -15^\circ}$$

Example 5: Determine V/Z

$$V = 100 - j50 \quad Z = 10 + j15$$

Soln:

$$V = 100 - j50 = 111.8 \angle -\tan^{-1} 0.5 = 111.8 \angle -26.6$$

$$Z = \cancel{11.8} 10 + j15 = 18.03 \angle \tan^{-1} 1.5 = 18.03 \angle 56.3^\circ$$

$$\frac{V}{Z} = \frac{111.8 \angle -26.6^\circ}{18.03 \angle 56.3^\circ} = 6.2 \angle -26.6 - 56.3$$

$$= 6.2 \angle -82.9^\circ$$

$$= 6.2 [\cos(-82.9^\circ) + j \sin(-82.9^\circ)]$$

$$= 6.2 \times 0.1236 + j 6.2 \times (-0.9923)$$

$$= \underline{7.66 - j 6.152}$$


Average and Effective Values of non-sinusoidal Waveforms

do it your self

have some practice of solving some problems.

Power and Power Factor

Let's consider

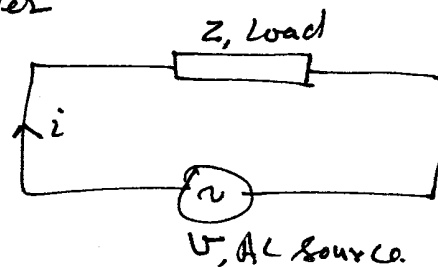

$$\begin{aligned} p &= vi = [V_m \sin \omega t] [I_m \sin (\omega t - \theta)] \\ &= V_m I_m \sin \omega t \sin (\omega t - \theta) \\ &= \frac{V_m I_m}{2} \left[\cos (\omega t - (\omega t - \theta)) - \cos (\omega t + \omega t - \theta) \right] \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \left[\cos \theta - \cos (2\omega t - \theta) \right] \\ &= VI [\cos \theta - \cos (2\omega t - \theta)] \\ &= \underbrace{VI \cos \theta}_{\text{Constant}} - VI \cos (2\omega t - \theta) \end{aligned}$$

The average value of 2nd term = 0

$$P = P_{av} = VI \cos \theta$$

$$P = \text{Real Power} = VI \cos \theta$$

$$VI = \text{Apparent power}$$

$$\cos \theta = \frac{P}{VI} = \frac{\text{real power}}{\text{Apparent power}}$$

In an inductive circuit I lags V and $\cos \theta$ is +ve
" " Capacitive " I leads V " " -ve
This is convention.

Example: In an electric network, the instantaneous voltage and current are given as

$$v = 55 \sin \omega t \quad \text{and} \quad i = 6.1 \sin (\omega t - \pi/5)$$

Determine P_{av} , P_a , p at $\omega t = 0.3$, p.f.

Soln:

$$\theta = \pi/5$$

$$V = \frac{55}{\sqrt{2}} = 38.89 \text{ V}$$

$$I = \frac{6.1}{\sqrt{2}} = 4.31 \text{ A}$$

$$\begin{aligned} P_{av} &= VI \cos \theta = 38.89 \times 4.31 \cos (\pi/5) \\ &= 167.62 \times 0.809 = \underline{135.6 \text{ W}} \end{aligned}$$

$$\begin{aligned} \text{Apparant power } P_a &= VI = 38.89 \times 4.31 \\ &= \underline{167.62 \text{ VA}} \end{aligned}$$


$$\begin{aligned} p &= VI \cos \theta - V \cdot I \cos (2\omega t - \theta) \\ &= 135.6 - 167.62 \cos (2 \times 0.3 - \pi/5) \\ &= 135.6 - 167.55 = \underline{-31.95 \text{ VA}} \end{aligned}$$

$$P_f = \cos \theta = \underline{0.809}$$

Steady State Response to Sinusoids

Resistive Circuit


Consider

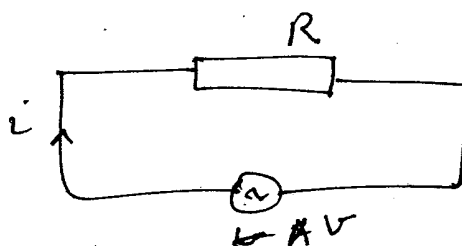

$$i = \frac{v}{R} \quad ; \quad I_m = \frac{V_m}{R} \quad ; \quad I = \frac{V}{R}$$

$$i = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t$$

I & V are in phase

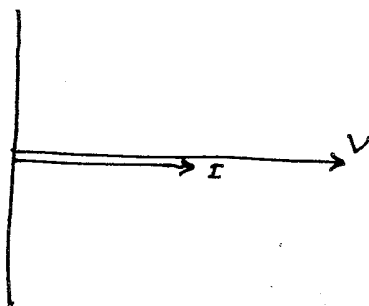


Inductive Circuit

$$i = I_m \sin \theta = I_m \sin \omega t$$

induced emf
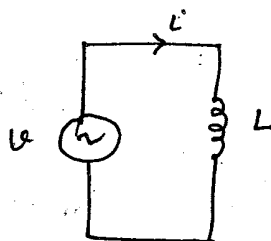
$$e = -L \frac{di}{dt} = -L \frac{d}{dt} (I_m \sin \omega t)$$



$$= -L I_m \omega \cos \omega t = -\omega L I_m \cos \omega t$$

$$= \omega L I_m \sin(\omega t - \pi/2)$$

So, ~~the~~ whole of the applied voltage v is absorbed in neutralizing the induced voltage e .

$$\therefore v = -e = \omega L I_m \cos \omega t = \omega L I_m \sin(\omega t + \pi/2)$$

\therefore Applied voltage leads the current by $\pi/2$

OR
Current lags the applied voltage by $\pi/2$



From above

$$V_m = \omega L I_m$$

$$\frac{V_m}{I_m} = \omega L = \frac{V}{I} = \text{Inductive reactance} \\ = X_L \Omega$$

$$X_L = \omega L = 2\pi f L$$

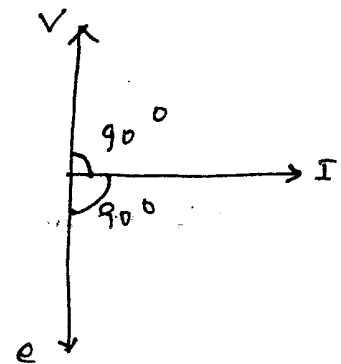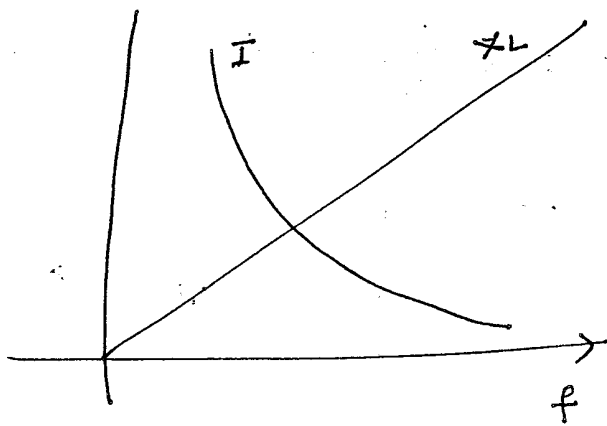
$$I = \frac{V}{X_L} = \frac{V}{2\pi f L}$$



Capacitive Circuit

$$i = C \frac{dv}{dt}$$
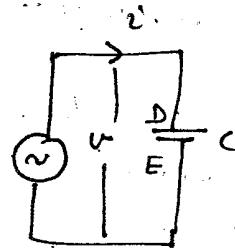
$$v = V_m \sin \omega t = \sqrt{2} V_m \sin \omega t$$





$$i = C \frac{dv}{dt} = C \cdot \frac{d}{dt} (V_m \sin \omega t)$$

$$= C V_m \omega \cos \omega t = \omega C V_m \cos \omega t$$

$$= \omega C V_m \sin(\omega t + \pi/2)$$
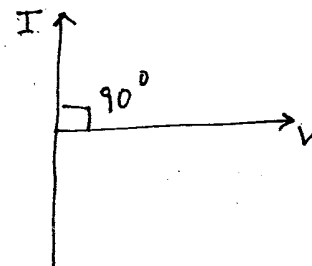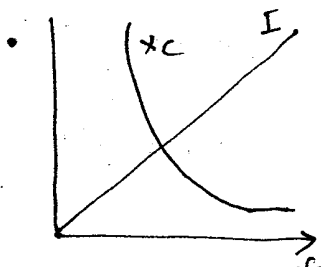
$$\frac{V}{I} = \frac{1}{\omega C} = \frac{1}{2\pi f C} = X_C = \text{Capacitive reactance}$$



Example: A $30\mu\text{F}$ capacitor is connected across a 400V , 50Hz supply. Calculate

(a) reactance of the capacitor


(b) current in the circuit.

Soln:


$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times \pi \times 50 \times 30 \times 10^{-6}}$$

$$= 106.2 \Omega$$
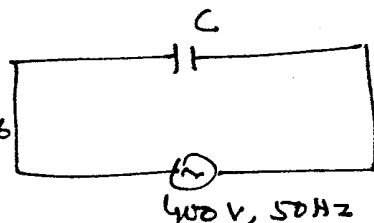
$$I = \frac{V}{X_C} = \frac{400}{106.2} = 3.77\text{A}$$





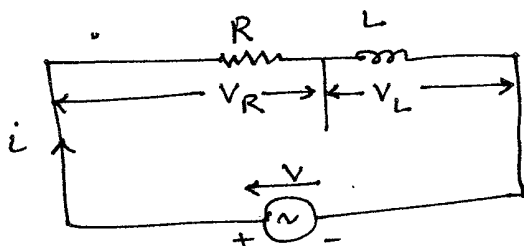
Series RL Circuit (reactive power + complex impedance)



$$\bar{V} = \bar{V}_R + \bar{V}_L$$

Bold letters means phasor in books.

\bar{V} here means phasor

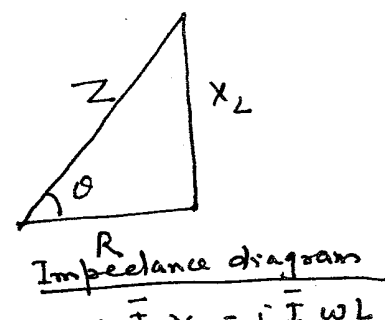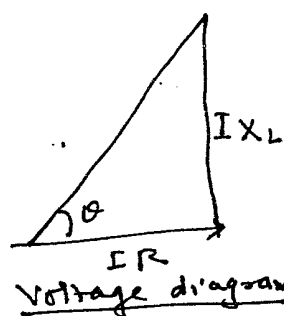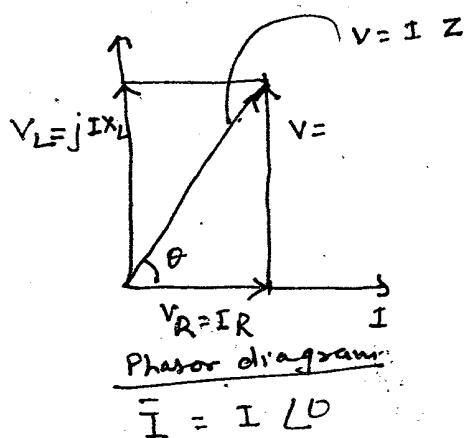

$$\bar{V}_R = \bar{I} R$$

$$\bar{V}_L = \bar{I} \cdot jX_L = j \bar{I} X_L = j \bar{I} \omega L$$

$$\bar{V} = \bar{I} R + j \bar{I} \omega L = \bar{I} (R + j \omega L)$$

$$\bar{I} = \frac{\bar{V}}{R + j \omega L} = \frac{\bar{V}}{\underline{Z}}$$


$$\bar{Z} = R + j\omega L$$

$$Z = \sqrt{R^2 + \omega^2 L^2} \quad \theta = \tan^{-1} \frac{\omega L}{R} = \sin^{-1} \frac{\omega L}{Z}$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{V \angle 0}{Z \angle \theta} = \frac{V}{Z} \angle -\theta \quad (\text{If } V \text{ is taken as reference})$$

Example : For the circuit shown below

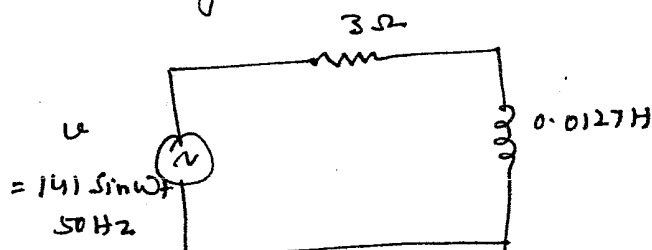- (i) Calculate the rms value of the steady state current as well as the reactive phase angle.
- (ii) Write the expression for the instantaneous current
- (iii) Find the average power dissipated in the circuit
- (iv) Calculate power factor
- (v) Draw the phasor diagram.



Soln:

$$(i) \quad \bar{V} = V \angle 0^\circ = \frac{V_m}{\sqrt{2}} \angle 0^\circ = \frac{141}{\sqrt{2}} \angle 0^\circ = 100 \angle 0^\circ$$

$$= 100 + j0$$

$$\bar{Z} = R + j\omega L = 3 + j2\pi f L = 3 + j2\pi \times 50 \times 0.0127$$

$$= 3 + j4 = 5 \angle 53.1^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{100 \angle 0^\circ}{5 \angle 53.1^\circ} = \underline{20 \angle -53.1^\circ} \text{ A}$$

effective value of current = 20 A
lags by the \bar{V} by 53.1° .


(ii)

$$i = \frac{20\sqrt{2} \sin(\omega t - 53.1^\circ)}{}$$


(iii)

$$P_{av} = VI \cos \theta = 100 \times 20 \times \cos(53.1^\circ) \\ = \underline{1200 \text{ W}}$$

$$(iv) \quad pf = \cos \theta = \cos(53.1^\circ) = \underline{0.6 \text{ lagging}}$$

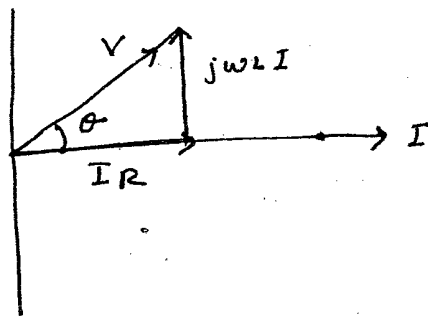(v) Phasor diagram

(A)

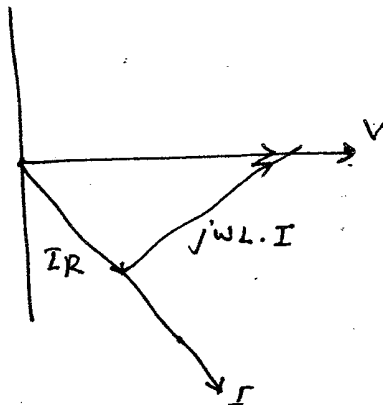

(B)

Reactive Power $VI = \text{Apparant Power}$ $VI \cos \theta = \text{Read Power}$

$$\text{If } \bar{V} = V \angle \theta \quad \text{and} \quad \bar{I} = I \angle \phi$$

$$P = VI \cos(\theta - \phi) = \text{Real power}$$

$$= VI \operatorname{Re} [e^{j(\theta - \phi)}] = \operatorname{Re} \left[\underbrace{(V e^{j\theta})}_I \underbrace{(I e^{-j\phi})}_{II} \right]$$

I factor $V e^{j\theta} = \text{phasor Voltage}$ II factor $I e^{-j\phi} = \text{complex conjugate of } \bar{I}$
 $= * \quad \angle -\phi$

Therefore,

$$P = \text{real power} = \operatorname{Re}[\bar{V} \bar{I}^*]$$

$$S = \text{Complex Power (VA)}$$

$$\bar{S} = \bar{V} \bar{I}^* = VI e^{j(\theta - \phi)}$$



$$= P + jQ$$

$$P = \text{Real Power (W)}$$

$$Q = \text{Reactive Power (VAR)}$$

$$Q = VI \sin(\theta - \phi)$$

Parallel RL Circuit

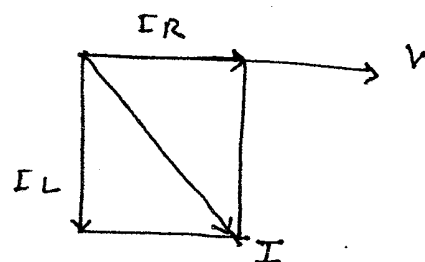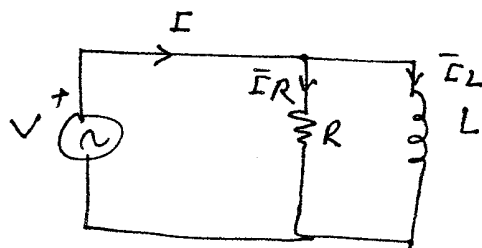

$$\bar{I}_R = \frac{\bar{V}}{R}, \quad \bar{I}_L = \frac{\bar{V}}{jX_L} = \frac{\bar{V}}{j\omega L}$$

$$\bar{I} = \bar{I}_R + \bar{I}_L = \bar{V} \left[\frac{1}{R} + \frac{1}{j\omega L} \right] = \bar{V} \bar{Y}$$

$$\bar{Y} = \text{Complex admittance} = \frac{1}{R} - j \frac{1}{\omega L}$$

$$= G + jB$$

$$G = \text{Conductance}$$

$$B = \text{Susceptance}$$

$$G = \frac{1}{R} \quad \text{and} \quad B = -\frac{1}{\omega L}$$

$$\bar{I} = \bar{V} \bar{Y} = \bar{V} (G + jB) = V \left(\frac{1}{R} - j \frac{1}{\omega L} \right)$$

$$\theta = \tan^{-1} \frac{-1/\omega L}{1/R} = \tan^{-1} \left(\frac{-R}{\omega L} \right)$$

Example: For $Z = 6 + j8$


Determine Conductance.

Soln.

$$\begin{aligned}
 Y &= G + jB = \frac{1}{Z} = \frac{1}{6 + j8} \\
 &= \frac{6 - j8}{(6 + j8)(6 - j8)} = \frac{6 - j8}{6^2 + 8^2} \\
 &= \frac{6 - j8}{100} = \frac{6}{100} - j \frac{8}{100} \\
 &= (0.06 - j 0.08) \text{ } \Omega^{-1}
 \end{aligned}$$

So $G = \underline{0.06 \text{ } \Omega^{-1}}$

Series RC Circuit

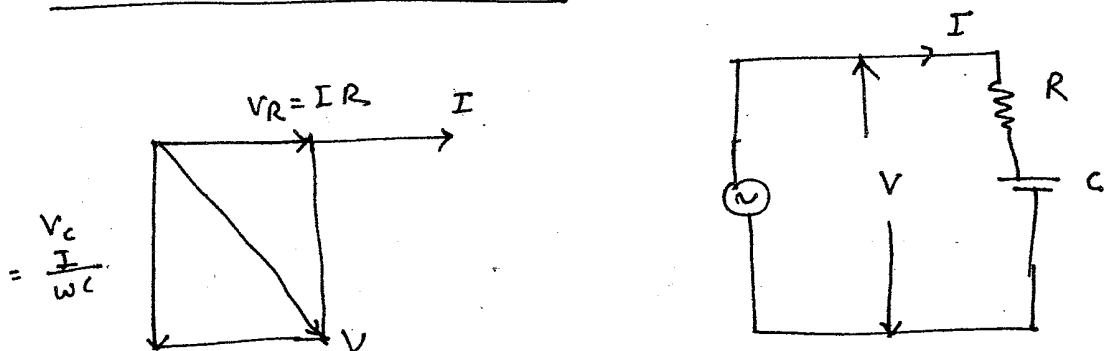

$$\bar{V} = \bar{I}R + I \left[\frac{1}{j\omega C} \right] = \bar{I} \left[R + \frac{1}{j\omega C} \right] = \bar{I} \bar{Z}$$

$$\bar{Z} = R - j \frac{1}{\omega C} = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \angle -\tan^{-1} \frac{1}{\omega CR}$$



$$\bar{I} = I \angle \theta = \frac{V \angle 0}{\sqrt{R^2 + 1/\omega^2 C^2}} \angle \tan^{-1} (1/\omega CR)$$

$$I = \frac{V}{\sqrt{R^2 + 1/\omega^2 C^2}} \quad \theta = \tan^{-1} (1/\omega CR)$$

$$i = I_m \sin(\omega t + \theta) = \frac{V_m}{\sqrt{R^2 + 1/\omega^2 C^2}} \sin(\omega t + \tan^{-1} (1/\omega CR))$$

Parallel RC Circuit

34

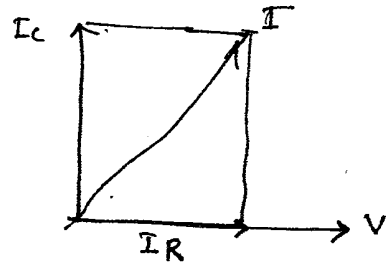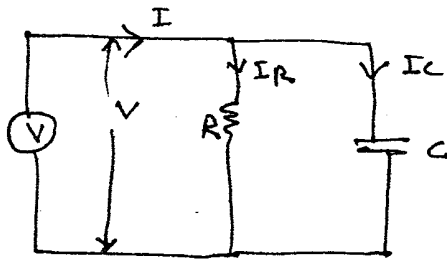

$$\bar{I}_R = \frac{\bar{V}}{R}$$

$$I_C = \frac{\bar{V}}{\frac{1}{j} \times C} = \frac{V}{1/j\omega C} = Vj\omega C$$

$$\bar{I} = \bar{I}_R + \bar{I}_C = \frac{\bar{V}}{R} + \bar{V}(j\omega C) = \bar{V} \left[\frac{1}{R} + j\omega C \right] = \bar{V} \bar{Y}$$


Admittance

$$\bar{Y} = \text{Complex Impedance} = G + jB$$

$$G = \frac{1}{R} \quad B = \omega C$$

$$\theta = \tan^{-1} \frac{B}{G} = \tan^{-1} \frac{\omega C}{1/R} = \tan^{-1} \omega CR$$

Series RLC Circuits

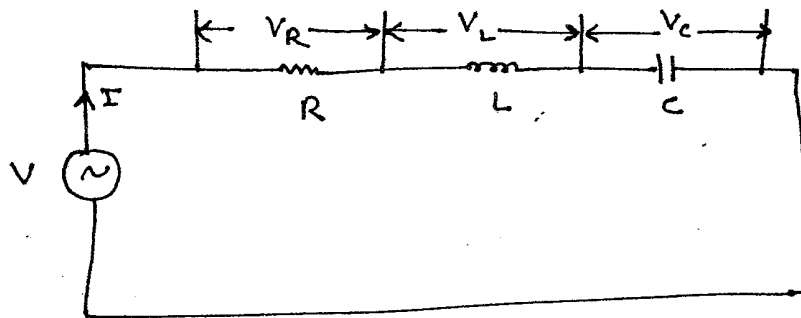

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C = \bar{I}R + \bar{I}(j\omega L) + \bar{I}(\frac{1}{j\omega C})$$

$$= \bar{I} \left[R + j\omega L + \frac{1}{j\omega C} \right] = \bar{I} \left[R + j \left(\omega L - \frac{1}{\omega C} \right) \right] = \bar{I} \bar{Z}$$

$$\bar{Z} = R + j \left[\omega L - \frac{1}{\omega C} \right] = \sqrt{R^2 + \left[\omega L - \frac{1}{\omega C} \right]^2} \angle \tan^{-1} \frac{(\omega L - 1/\omega C)}{R}$$

$$\bar{I} = I \angle \theta = \frac{V \angle 0^\circ}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \angle -\tan^{-1} \frac{(\omega L - 1/\omega C)}{R}$$

$$i = \sqrt{2} I \sin(\omega t + \theta)$$




$$I = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} ; \theta = -\tan^{-1} \frac{(\omega L - \frac{1}{\omega C})}{R}$$


\bar{I} may lag, lead or in phase with V

(a) $\omega L > \frac{1}{\omega C}$ θ is -ve \bar{I} lags \bar{V}

(b) $\omega L < \frac{1}{\omega C}$ θ is +ve \bar{I} leads \bar{V}


(c) $\omega L = \frac{1}{\omega C}$ $\theta = 0$ \bar{I} in phase with \bar{V}
(Resonance)

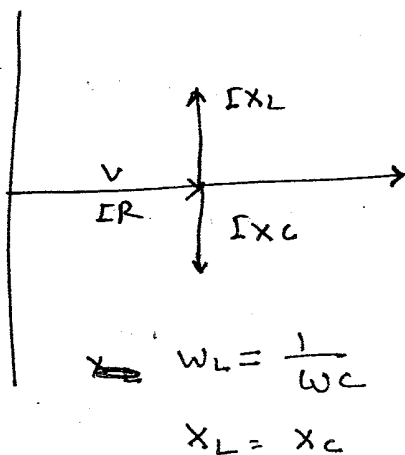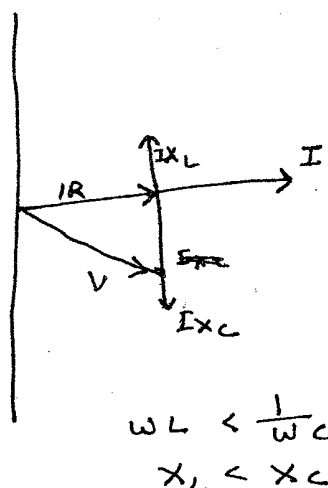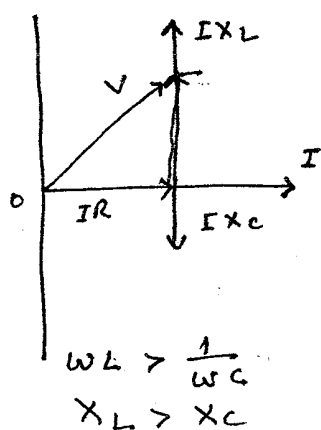

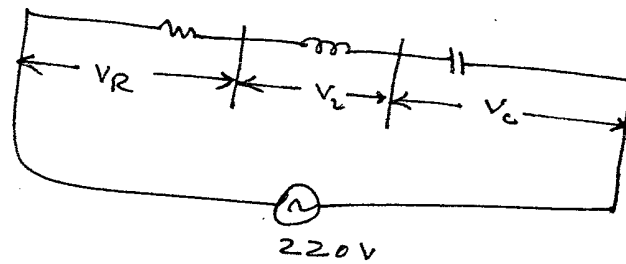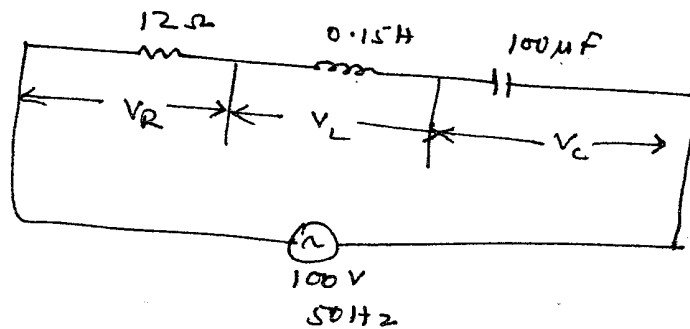Example 1

Given $V_L = 50\text{ V}$ $V_C = 50\text{ V}$ Find $V_R = ?$

Soln: $V_R = 220\text{ V}$

Example 2

Calculate:

- (a) impedance (b) current (c) V_R, V_L & V_C
 (d) phase difference between \bar{V} and \bar{I}

Soln:

(a) $R = 12\ \Omega$

$$X_L = \omega L = 2\pi f L = 2\pi \times 50 \times 0.15 = 47.1$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.85$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{12^2 + (47.1 - 31.85)^2} = 19.4\ \Omega$$

(b) $I = \frac{V}{Z} = \frac{100}{19.4} = 5.15\text{ A}$

(c)

$$V_R = IR = 5.15 \times 12 = 61.8\text{ V}$$

$$V_L = I X_L = 5.15 \times 47.1 = 242.5\text{ V}$$

$$V_C = I X_C = 5.15 \times 31.85 = 164.0\text{ V}$$

(d) Phase difference between \bar{V} and \bar{I}

$$\phi = \cos^{-1} \frac{VR}{V} = \cos^{-1} \left[\frac{61.8}{100} \right] = 51^\circ 50'$$

Also

$$\phi = \tan^{-1} \frac{(X_L - X_C)}{R} = \tan^{-1} \frac{(47.1 - 30.85)}{12}$$

$$= \tan^{-1} 1.271 = 51^\circ 50'$$

Since $X_L > X_C$ \bar{I} lags \bar{V} .

Resonance in Series Circuits

Definitions

1. Circuit p-f. is unity.
2. \bar{V} and \bar{I} are in phase.
3. X is zero.
4. B is zero.

Consider the circuit at p-36

$$Z = R + jX_L - jX_C = R + j(X_L - X_C)$$

$$\text{If } X_L - X_C = 0 \Rightarrow \text{resonance}$$

The conditions of resonance are represented as

$$f_0, Z_0, X_{C0}, X_{L0}$$

Therefore: At Resonance

$$X_{L0} - X_{C0} = 0$$

$$X_{L0} = X_{C0}$$

$$2\pi f_0 L = \frac{1}{2\pi f_0 C}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

~~$$Z_0 = R + j\omega L$$~~

$$Z_0 = R + j\omega L \quad \& \quad I_0 = \frac{V}{R}$$

and

$$V_R = I_0 R = \frac{V}{R} R = V$$

$$V_L = I_0 X_{L_0} = \frac{V}{R} X_{L_0} = V \frac{X_{L_0}}{R} = VQ \quad \left\{ \begin{array}{l} n \\ s \end{array} \right.$$

$$V_C = I X_{C_0} = \frac{V}{R} X_{C_0} = V \frac{X_{C_0}}{R} = VQ$$

But, $X_{L_0} = X_{C_0}$

$$\therefore V_L = V_C \quad \text{and} \quad V_R = V$$

Quality Factor (of a coil)

- It is measure of effectiveness of a coil
- It is ~~also~~ defined as ratio of energy stored to the energy dissipated per cycle.

$$Q = \frac{\text{Stored Power}}{\text{Dissipated power}} = \frac{I^2 X_L}{I^2 R} = \frac{X_L}{R} = \tan \phi$$

$$I^2 X_L = \text{Reactive Power in the coil} \\ = \text{Power stored}$$


→ Here R means the resistance of the coil and ~~not~~ ^{may/may not} ~~doesn't~~ include any resistance outside the coil.

- Quality factor is used as a figure of merit for the coil
- ↑ Q means better coil.
 - $Q < 10$ low-Q-coils
 - $Q > 10$ high-Q-coils
 - $Q \approx 200-300$ are used in electronic circuits.

Comments: If Q of a coil is

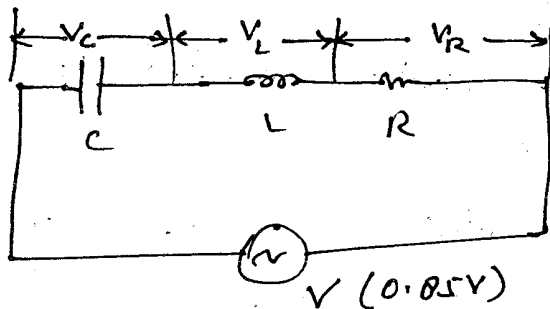Example: The voltage applied to the series circuit given below. The Q of the coil is 50 and the value of capacitor is 320 pF . The resonant frequency is 175 kHz . Find:

- L
- Current in circuit
- Voltage across capacitor under resonance
- Draw phasor diagram.



Soln:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$L = \frac{1}{(2\pi)^2 \cdot C \cdot f_0^2}$$

$$= \frac{1}{4(\pi^2) \cdot 320 \times 10^{-12} \times (175)^2} = \underline{2.58 \text{ mH}}$$


$$X_{L0} = X_{C0} = 2\pi f_0 L = 2\pi (175 \times 10^3) \times 0.00258 \\ = 2836.85 \Omega$$

$$R = \frac{X_{L0}}{Q} = \frac{2836.85}{50} = \underline{56.74 \Omega}$$


~~Z of~~ $Z_0 = (56.74 + j0) \Omega$

$$I_0 = \frac{V}{R} = \frac{0.85}{56.74} = 0.01498 \text{ A} = \underline{14.98 \text{ mA}}$$
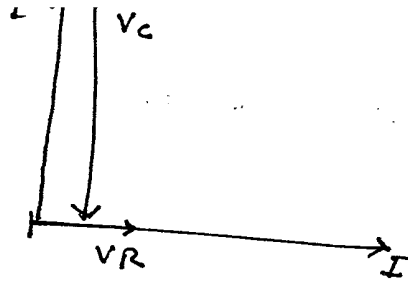
$$V_L = QV = 50 \times 0.85 = 42.5 \text{ V} = V_L$$



Effects of Variation of Frequency

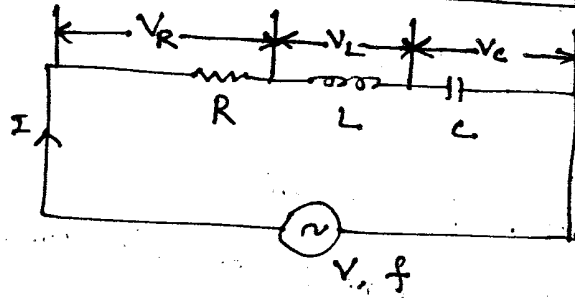

Let R, L, C , and V are fixed
 f is variable


Purpose, here is to study variation of X_L and X_C with frequency

$+j$ is associated with X_L , X_L is taken as $+ve$
 $-j$ " " " X_C , X_C " " $-ve$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

Net reactance $X = X_L - X_C$

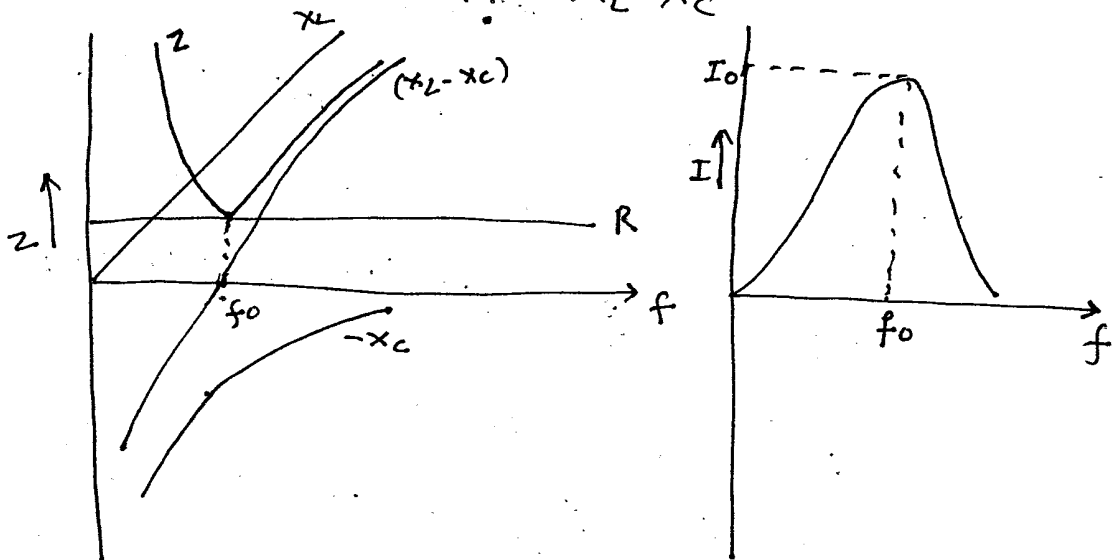

at $f < f_0$ circuit is capacitive I leads V
 $f > f_0$ " " Inductive I lags V
 $f = f_0$ " " Resistive. I in phase with V

$$\bar{Z} = \sqrt{R^2 + (X_L - X_C)^2} \angle \tan^{-1} \frac{X_L - X_C}{R}$$

$$\bar{Z}_0 = R + j0 = R$$

$$I_0 = \frac{V}{Z_0} = \frac{V}{R}$$

I is maximum at f_0

Next,

consider f_1 and f_2 where

$$|X_L - X_C| = R$$

At f_1 circuit is capacitive $X_L - X_C = -R$

f_2 " " Inductive. $X_L - X_C = R$

Now, the impedances at f_1 and f_2

$$Z_1 = \sqrt{R^2 + (-R)^2} \angle \tan^{-1} \frac{-R}{R} = \sqrt{2} R \angle -45^\circ$$

$$Z_2 = \sqrt{R^2 + R^2} \angle \tan^{-1} \frac{R}{R} = \sqrt{2} R \angle 45^\circ$$

Currents

$$I_1 = \frac{V}{\sqrt{2} R \angle -45^\circ} = \frac{V}{\sqrt{2} R} \angle 45^\circ = 0.707 I_0 \angle 45^\circ$$

$$I_2 = \frac{V}{\sqrt{2} R \angle 45^\circ} = \frac{V}{\sqrt{2} R} \angle -45^\circ = 0.707 I_0 \angle -45^\circ$$

This means at f_1 as well as f_2 the current falls to $0.707 I_0$. This concept can be used to define Bandwidth.

$$BW = f_2 - f_1$$

f_1 = lower cut-off frequency

f_2 = upper cut off frequency


- At f_1 and f_2 current reduces to $I_0/\sqrt{2}$

$$P_0 = I_0^2 R$$

$$P_1 = \left(\frac{I_0}{\sqrt{2}}\right)^2 R = \frac{I_0^2}{2} R = P_0/2$$


$$P_2 = \left(\frac{I_0}{\sqrt{2}}\right)^2 R = \frac{I_0^2}{2} R = P_0/2$$

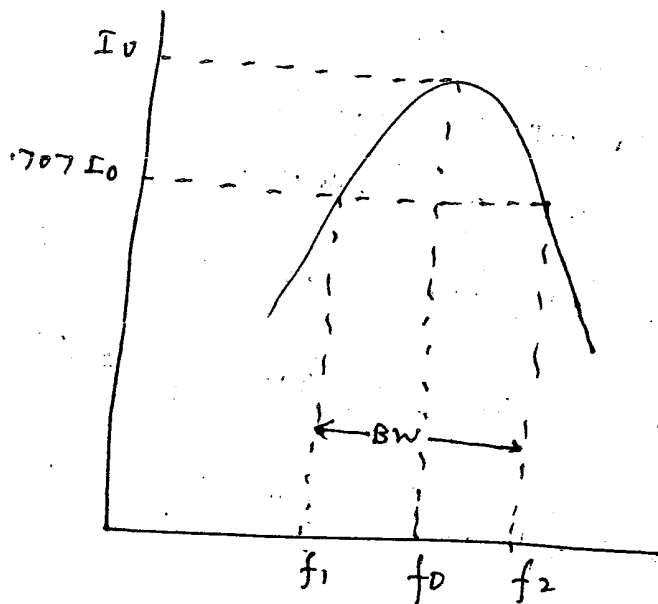So, f_1 and f_2 are also known as half power frequencies.



Resonance in Parallel AC Circuits

Consider:

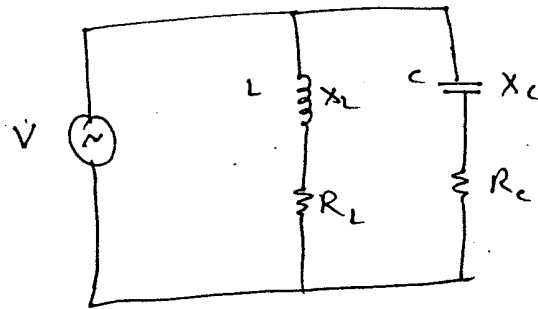

$$\bar{X}_C = \frac{1}{j\omega C} \\ = -j\left(\frac{1}{\omega C}\right)$$

$$Z_L = R_L + jX_L \quad Y_L = \frac{1}{R_L + jX_L}$$

$$Y_L = \frac{R_L - jX_L}{(R_L + jX_L)(R_L - jX_L)} = \frac{R_L - jX_L}{R_L^2 + X_L^2}$$

And

$$Z_C = R_C - jX_C \quad Y_C = \frac{1}{R_C - jX_C}$$

$$Y_C = \frac{R_C + jX_C}{(R_C - jX_C)(R_C + jX_C)} = \frac{R_C + jX_C}{R_C^2 + X_C^2}$$

$$Y_T = \cancel{Y_L} + Y_L + Y_C = \frac{R_L - jX_L}{R_L^2 + X_L^2} + \frac{R_C + jX_C}{R_C^2 + X_C^2}$$

Collecting the real and imaginary terms.

$$Y_T = \left[\frac{R_C}{R_C^2 + X_C^2} + \frac{R_L}{R_L^2 + X_L^2} \right] + j \left[\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right]$$

At resonance the reactance part (j part) = 0

$$\therefore \frac{X_{C0}}{R_C^2 + X_{C0}^2} - \frac{X_{L0}}{R_L^2 + X_{L0}^2} = 0$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - (L/C)}{R_C^2 - (L/C)}}$$

- In most of the applications C can be considered lossless i.e. $R_C = 0$.
- If it is so.


$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - (L/C)}{-L/C}} = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - R_L^2 C/L}$$

If R_L is also $= 0$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

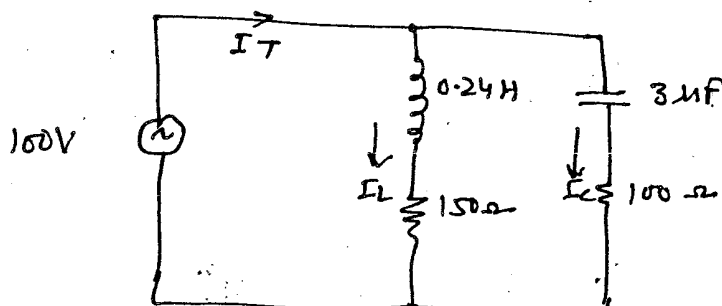Example: For the circuit given below, determine

- Source current \bar{I}_T
- input impedance \bar{Z}_T



Soln:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - (L/C)}{R_C^2 - (L/C)}} = \underline{170 \text{ Hz}}$$

$$X_{L0} = 2\pi f_0 L = 2\pi \times 170 \times 0.24 = 256 \Omega$$

$$X_{C0} = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 170 \times 3 \times 10^{-6}} = 312 \Omega$$

$$\bar{I}_L = \frac{V}{R_L + jX_{L0}} = \frac{100}{150 + j256} = (0.170 - j0.291) \text{ A}$$


(do it on calculator & report now)

$$\bar{I}_C = \frac{V}{R_C - jX_{C0}} = \frac{100}{100 - j312} = (0.093 + j0.291) \text{ A}$$

Total current

$$\begin{aligned}\bar{I}_T &= \bar{I}_L + \bar{I}_C = (0.170 - j0.291) + (0.0393 + j0.291) \\ &= (0.263 + j0) \text{ A} =\end{aligned}$$
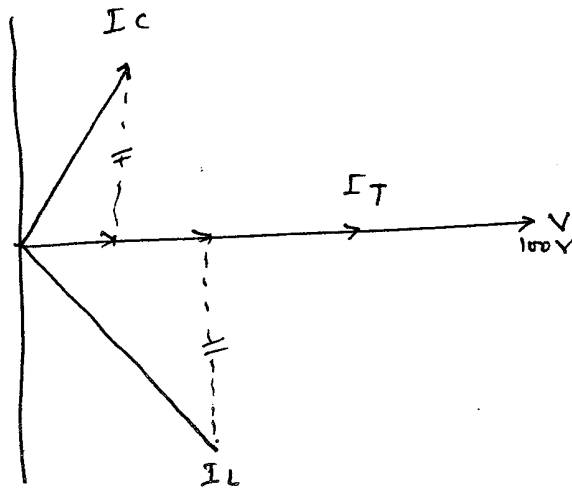
$$\bar{Z}_T = \frac{V}{I_T} = \frac{100}{0.263 + j0} = \underline{(380 + j0) \text{ A}}$$



Example: