

# Experiment No.:- 02

1) Aim:- To verify Thevenin's Theorem

2) Apparatus:- Wires, D.C sources, Resistances, Ammeter, Voltmeter

3) Theory:- It provides a mathematical technique for replacing a given network, as viewed from two terminals, by a single voltage source with a series resistance. It makes the solution of complicated networks quite quick and easy. The application of this extremely useful theorem will be explained with the help of following simple example

Suppose, it is required to find current flowing through Load Resistance  $R_L$ , as shown in diagram.


This expression proceed as follows:-

- 1) Remove  $R_L$  from the circuit terminals A and B and redraw the circuit as shown in diagram. Obviously the terminal have become open circuit.


## Experiment No: 2.

Aim: To verify Thevenin's Theorem.

Circuit diagram:

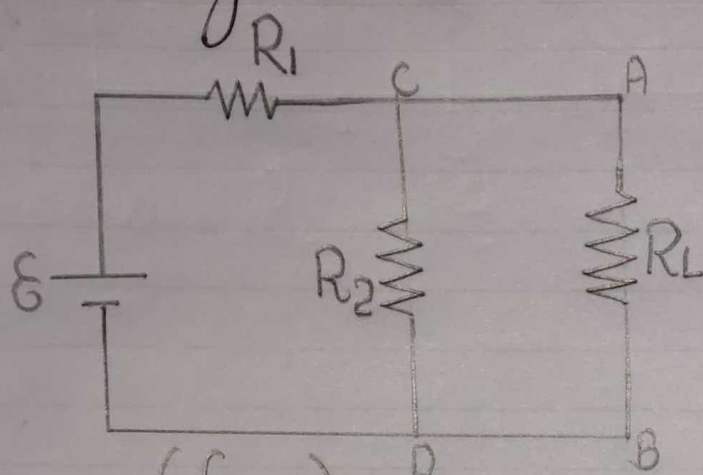

(fig i)

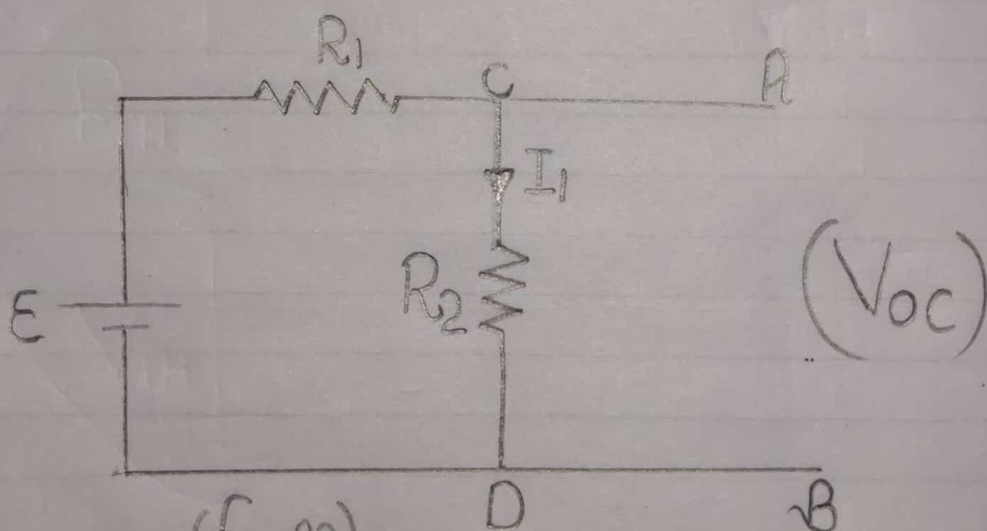

(fig ii)



- 2) Calculate the open circuit voltage ( $V_{oc}$ ) which appears across terminals A and B when they're open i.e. when  $R_L$  is removed.

As seen,  $V_{oc} = \text{drop across } R_2 \Rightarrow IR_2$  where  $I$  is the circuit current when A and B is open  $\therefore$

$$I = \frac{E}{r + R_1 + R_2}$$


$$V_{oc} = IR_2$$

$$V_{oc} = \left( \frac{E}{r + R_1 + R_2} \right) R_2$$


It is also called Thevenin's voltage

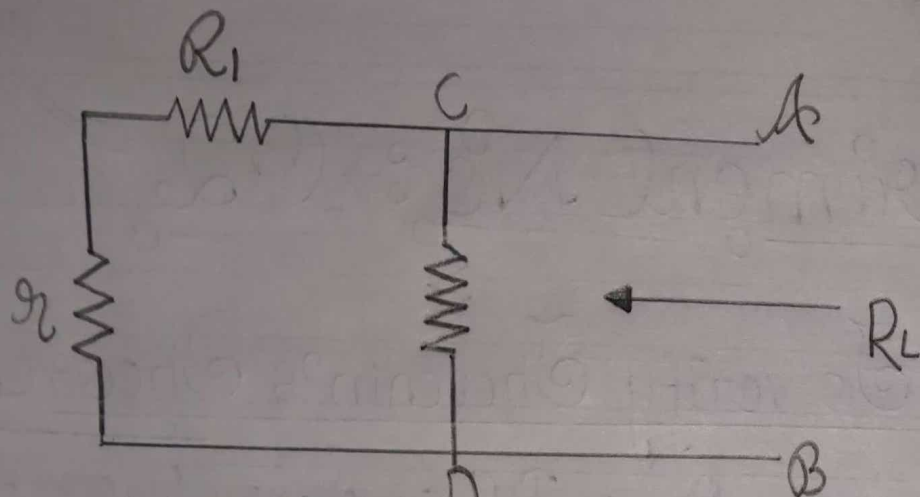- 3) Now imagine the battery to be removed from the circuit, leaving its internal resistances  $r$  behind and redraw the circuit as shown in diagram. When viewed inwards from the terminals A and B, the circuit consists of two parallel paths one containing  $R_2$  and another containing  $(R_1 + r)$ . The equivalent resistance of the network as viewed from these network's terminals is given as

$$\left( \frac{(R_1 + r)R_2}{R_1 + r + R_2} \right) = R_{TH}$$



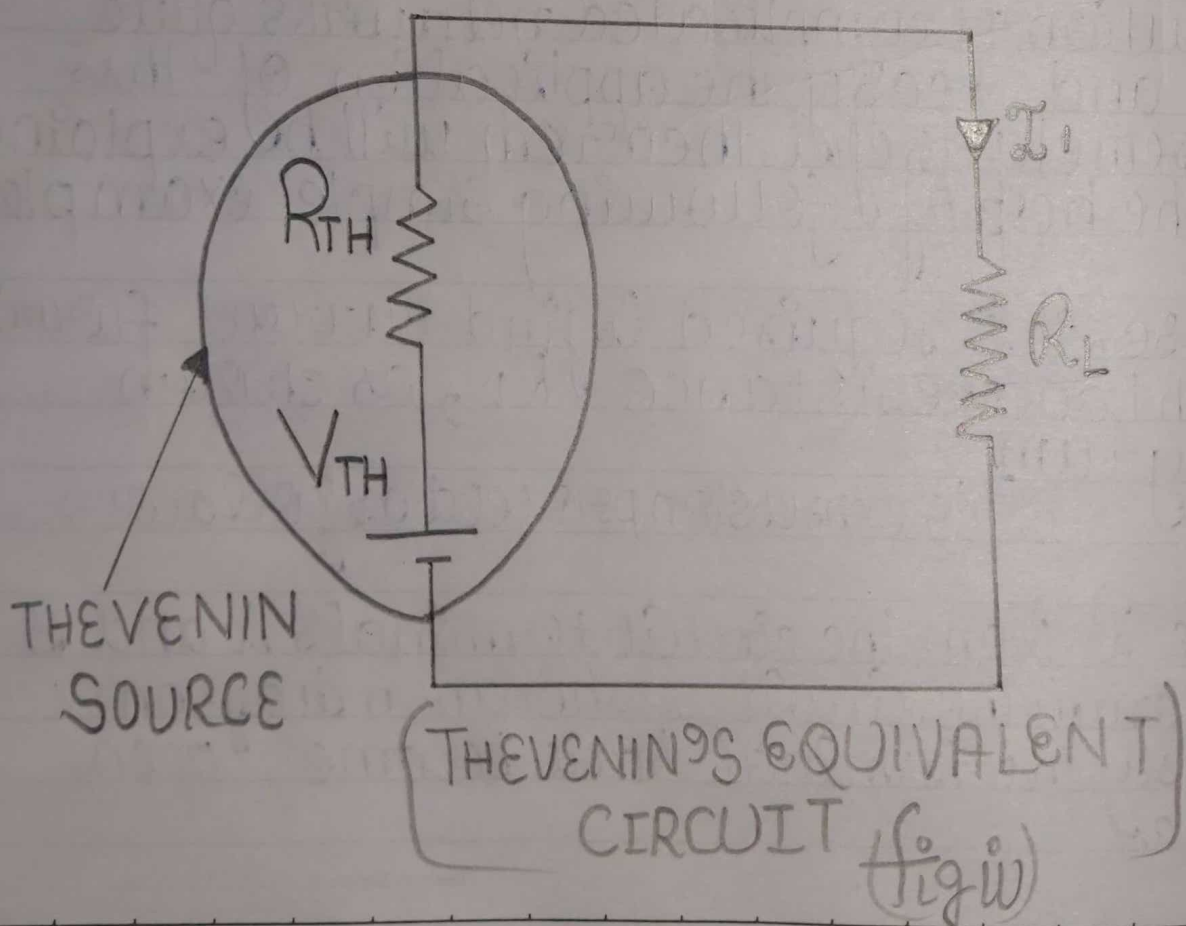Circuit with  $R_L$  and  $E$  removed (fig iii)





The resistance is called Thevenin's Equivalent Resistance.


Consequently as viewed from terminals A and B, the whole network (excluding  $R_L$ ) can be reduced to single source (called Thevenin's source) whose emf is equal to  $V_{oc}$  and whose internal resistance is equal to  $R_{TH}$  as shown in diagram

$R_L$  is now connected back across terminals A and B from where it was temporarily removed earlier. Current flowing through  $R_L$  is given by: 
$$\frac{V_{TH}}{R_{TH} + R_L}$$

#### 4) Procedure:-

1) Keep all the resistances close to their maximum respective values

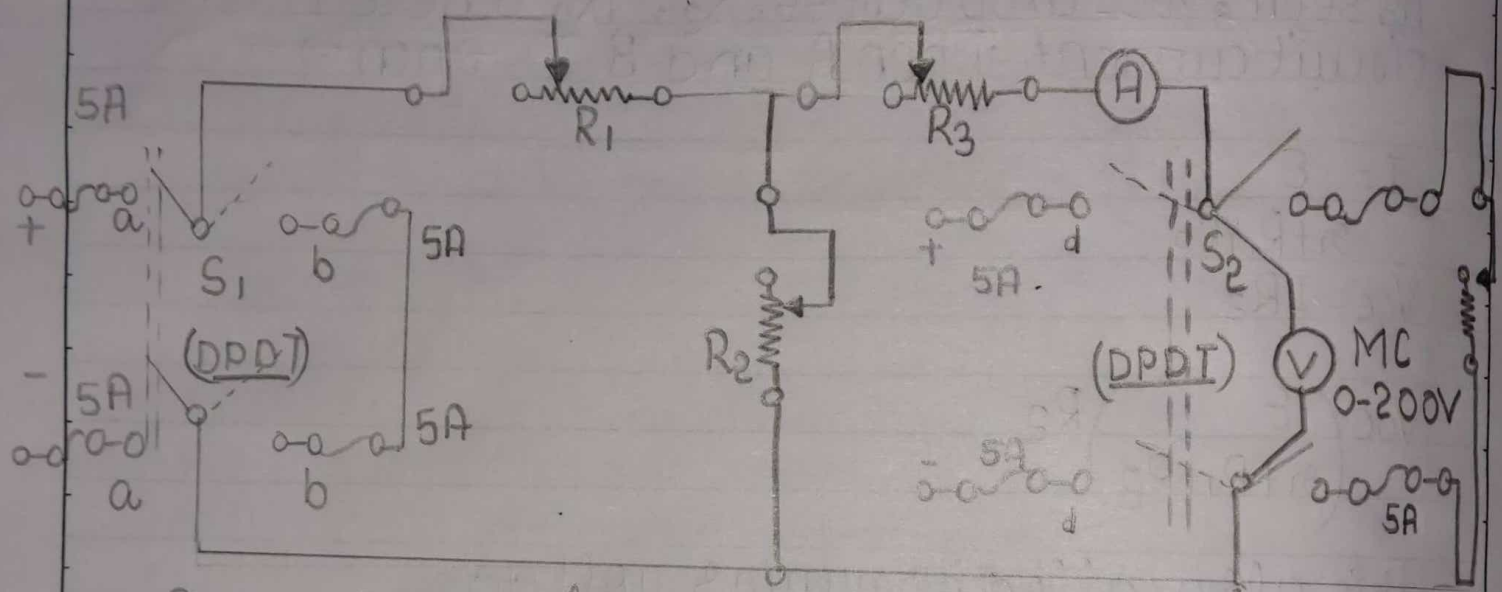2) Close the switch  $S_1$  to "aa" and  $S_2$  to "cc" positions. Observe the Load current ( $I_L$ ) and Voltage ( $V_L$ ) readings. The Load resistance 
$$R_L = \left( \frac{V_L}{I_L} \right)$$



Circuit diagram for experimental set up for verification of Thevenin's Theorem



The resistance is called Thevenin's Equivalent Resistance.

Consequently as viewed from terminals A and B, the whole network (excluding  $R_L$ ) can be reduced to single source (called Thevenin's source) whose emf is equal to  $V_{oc}$  and whose internal resistance is equal to  $R_{TH}$  as shown in diagram

$R_L$  is now connected back across terminals A and B from where it was temporarily removed earlier. Current flowing through  $R_L$  is given by: 
$$\left( \frac{V_{TH}}{R_{TH} + R_L} \right)$$

#### 4) Procedure:-

- 1) Keep all the resistances close to their maximum respective values
- 2) Close the switch  $S_1$  to "aa" and  $S_2$  to "cc" positions. Observe the Load current ( $I_L$ ) and Voltage ( $V_L$ ) readings. The Load resistance 
$$R_L = \left( \frac{V_L}{I_L} \right)$$

3) Remove the load by opening the switch  $S_2$  and read the open circuit voltage (or Thévenin equivalent voltage)  $V_{TH}$

4) Next, compute the resistance ( $R_{TH}$ ) of the network as seen from the load terminals.

4) Replace the 220 V source by a short by closing  $S_1$  to "bb". Apply 110 V at the output terminals by closing  $S_2$  to "dd". Read the voltmeter and ammeter (1) and get

$$R_{TH} = V/I$$

5) Now compute the load current, Applying Thévenin theorem

$$\left( \frac{V_{TH}}{R_{TH} + R_L} \right)$$

6) Compare the above computed load current with its observed value in step (2) & verify the theorem

Case 1:-> Circuit analysis of to determine load current (14)



To get the load current, select switches  $S_1$  to Power and  $S_2$  to load. And then click on Simulate. We will get the value of load current  $I_L$  from Case 1 tab.

Case 2: Thevenin Voltage Analysis :->

Apply switch  $S_1$  to power and  $S_2$  to intermediate. Simulate the program. Read Thevenin voltage ( $V_{TH}$ ) from Case 2 Tab. Read.

Thevenin Resistance analysis

Apply switch  $S_1$  to short and  $S_2$  to power. Simulate the program. Read Thevenin Resistance ( $R_{TH}$ ) from case 2 tab.

Case 3: Using  $V_{TH}$  and  $R_{TH}$  to determine the load current.

Click on Simulate to get the Load current ( $I_L$ ) from the Thevenin experiment equivalent parameters of the above circuit. Compare the load currents ( $I_L$ ) obtained in this case from Case 1. & fill data to the observation table.

S.no of observ ation	Load Current ( $I_L$ ) from case	Load voltage ( $V_L$ )	Load Resistance $R_L = V_L / I_L$	Thevenin voltage ( $V_{th}$ ) from case 2a	2nd Voltage source ( $V$ ) for case 2b	Ammeter Reading ( $I$ ) from case 2	Thevenin Resistance $R_{th} = V / I$	Load current $I_L = \frac{V_{th}}{R_{th} + R_L}$
1	0.10645	53.225	500	82.500	220	0.80000	275.00	0.10645
2	0.10924	54.620	500	85.549	225	0.79474	283.11	0.10924
3	0.11124	56.1762	505	88.571	230	0.78986	291.19	0.11124
4	0.11315	57.7065	510	91.570	235	0.78531	299.24	0.11315
5	0.11498	59.2147	515	94.545	240	0.78107	307.27	0.11498
	Case 1			(Case 1 = Case 3) Hence Proved				Case 3



Result  $\Rightarrow$  The Thevenin's Theorem has  
been verified as the results from the observation  
on Table are Identical. Ans.