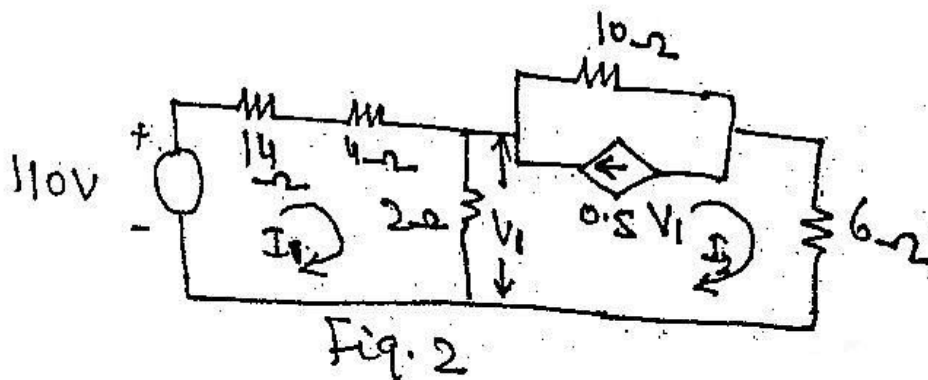



3[a] Find currents I_1 and I_2 in the circuit shown in Fig.2

7



[b] Obtain a Thevenin's equivalent at terminals a-b for the circuit shown in Fig.3

7

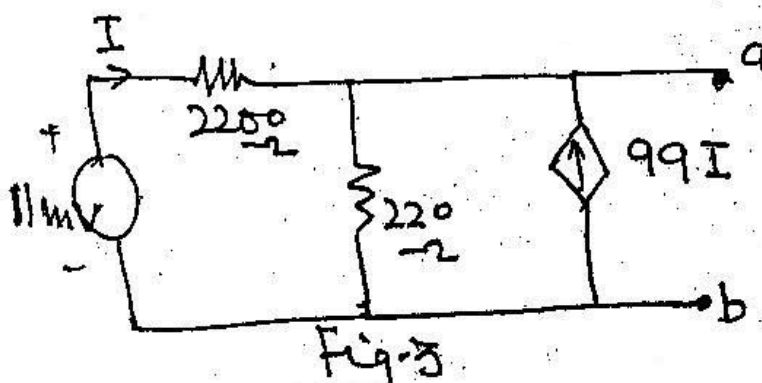

4[a] An alternative voltage $(80 + j 60)$ V is applied to a circuit and the resulting current flowing in the circuit is $(-4 + j 10)$ A. Find (i) Impedance and admittance of the circuit (ii) Power consumed (iii) Phase angle (iv) Resistive and reactive components. (v) Apparent power.

7

[b] Two impedances z_1 and z_2 are connected in parallel. The first branch takes a leading current of 16 A and has a resistance of 6Ω , while second branch takes a lagging current at power factor 0.8. The total power is 5 kW. The applied voltage being $(100 + j 200)$ V. Determine : (i) Circuit constant of the network (ii) branch currents (iii) total current.

7

- 5[a] In a series RLC a circuit consisting of $R = 2\Omega$, $L = 1\text{mH}$ and $C = 0.4\ \mu\text{F}$. Find (i) resonance frequency
 (ii) Half power frequencies
 (iii) Quality factor
 (iv) Bandwidth
 (v) Amplitude of currents at ω_0 , ω_1 and ω_2 if applied voltage is $20\sin\omega t$


10

- [b] Explain the principle of operation of 3-phase induction motor.

4

- 6[a] Calculate the power supplied to the 10Ω resistor in the ideal transformer shown in Fig.4

10

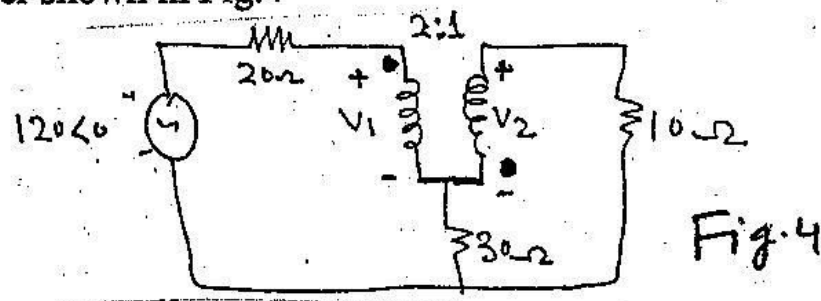

- [b] Compare electrical and magnetic quantities.


4

- 7 Efficiency of 400/200V, 200 kVA single phase transformer is 98.5% at full load at 0.8 pf lagging. At half load and at 0.8 pf lagging the efficiency is 97.5% calculate the values of core loss and copper loss at full load.

7

- [b] Consider the circuit in Fig.5 determine coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ sec if $V = 60 \cos(4t + 30^\circ)$ volt

7

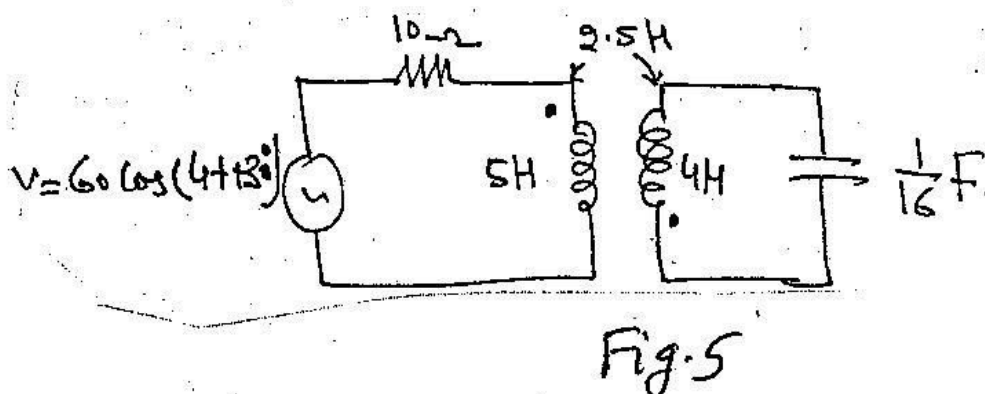

8[a] A star connected 3-phase load has a resistance of 8Ω and inductance 0.0191H in each phase. It is fed from 400V , 50 Hz , 3-phase balanced supply. Determine

- i. Line currents in all phases
- ii. Power factor
- iii. Power
- iv. Apparent power
- v. If power is measured by two wattmeter method. Determine W_1 and W_2
- vi. Draw neatly phasor diagram.

10

[b] Discuss advantages of digital instruments.

4

EE-105 ELECTRICAL SCIENCES

Time: 3 Hours

Maximum Marks : 70

Note: Question No. **ONE** is compulsory.
 Answer any **FOUR** questions from the remaining.
 Assume suitable missing data, if any

- 1[a] Explain main features of dependent sources and independent sources.
 [b] Show that Norton theorem and Thevenin's theorem are dual to each other.
 [c] Show that for a parallel RLC circuit $f_0^2 = f_1 \cdot f_2$, where f_0 , f_1 and f_2 are frequencies at resonance and half power points.
 [d] While measuring power in a 3 phase circuit by two wattmeter method one of the wattmeters indicates a negative reading explain the reasons.
 [e] An induction motor of the same rating that of 3- ϕ transformer, draws more current at no load than a transformer. Explain with justification.
 [f] Why is eddy current damping not provided in moving iron instruments?
 [g] Explain the significance of BH curve.
- 7×2=14
- 2[a] Draw V-I characteristics of the following (i) Ideal voltage and current sources (ii) Ohmic and non-ohmic elements. 4
 [b] The current in a 10 Henry inductor is shown in Fig.1. Sketch wave forms for the voltage $v(t)$, the instantaneous power $p(t)$ and the energy stored $w(t)$ as a function of time. 10

