


## EE-105 ELECTRICAL SCIENCES

Time: 1 Hour 30 Minutes

Max. Marks : 20

Note : Answer **ALL** questions.  
Assume suitable missing data, if any.

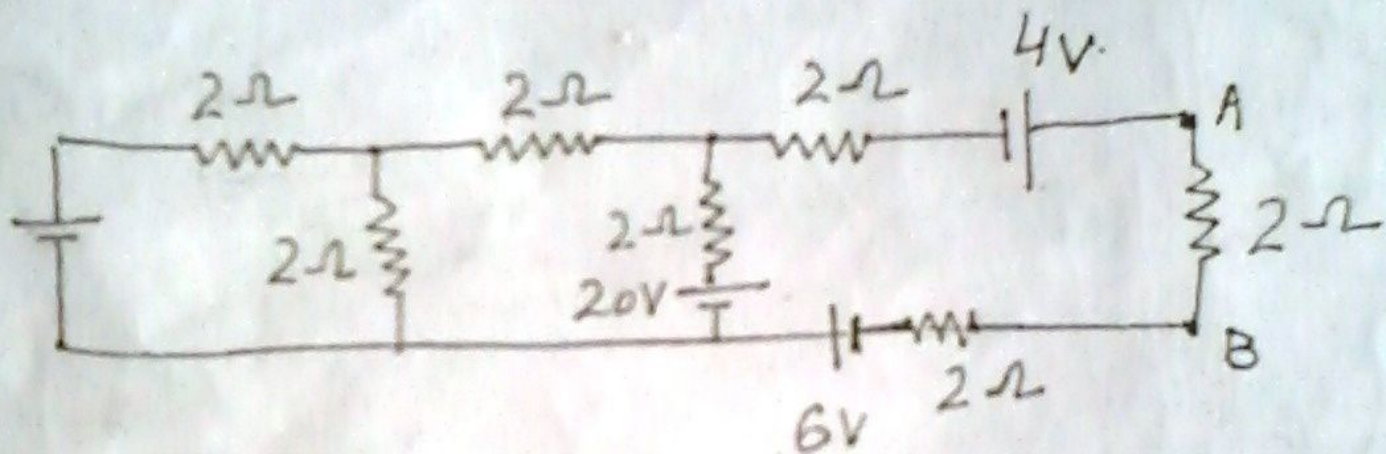- 1[a] State and explain Tellegen's theorem (two statements) with example. 2
- [b] Determine the current through the resistance of  $2\Omega$  connected across AB, using Thevenin's theorem, shown in Fig.1 4



- 2[a] A potential difference of  $100 + 200\sqrt{2} \sin 314t$  is applied to a circuit having a resistance of  $10\Omega$  in series with a reactance of  $15.7\Omega$ . Find the power expended and the impedance and power factor of the circuit. 3
- [b] A coil of  $20\Omega$  resistance has an inductance of  $0.2H$  and is connected in parallel with  $100\mu F$  capacitor. Calculate the frequency at which the circuit will act as a non-inductive resistance of ' $R$ ' ohms. Find also the value of  $R$ . 3
- 3[a] An electric iron is marked  $230V, 500W$ . What current does it take if connected to the  $200V$  voltage source? What is hot resistance? If the iron is used for one hour daily for 30 days in a month, what will be the monthly bill at Rs. 4.50 per unit, if the iron is connected to (i)  $230V$  and (ii)  $200V$  respectively? 3



ed as  
e of the current in each branch  
ge.

