

**DELHI TECHNOLOGICAL
UNIVERSITY
BEE LAB**



EXPERIMENT NO 5

**TO VERIFY THE
TELLENGEN'S THEOREM**

**PARTH
JOHRI
2K20/B17/33**

AIM :- To Verify Tellegen's Theorem.

THEORY :-

According to **Tellegen theorem**, the summation of instantaneous powers for the n number of branches in an electrical network is zero.

In any network the *algebraic sum of power at any given point is zero.*

We can say that,

Power delivered by some elements = Power absorb by the remaining elements.

Note:

1.) It depends on voltage and current product of an element but not on the type of element.

2.) While verifying Tellegen's theorem do not disturb original network

Suppose there are 'n' number of branches in an electrical network have $i_1, i_2, i_3, \dots, i_n$ respective instantaneous currents through them. These currents satisfy **Kirchhoff's Current Law**.

Again, suppose these branches have instantaneous voltages across them are $v_1, v_2, v_3, \dots, v_n$ respectively. If these voltages across these elements satisfy **Kirchhoff Voltage Law** then,

v_k is the instantaneous voltage across the k^{th} branch and i_k is the **instantaneous** current flowing through this branch. **Tellegen theorem** is applicable to lumped networks that consist of **linear, non-linear, time variant, time-invariant,** and **active and passive elements.**

Thus, this **theorem states that:**

For k^{th} source :-

$$\sum_{K=1}^n v_K i_K = 0$$



Where ,

n is the number of branches

v_K is the voltage in the branch

i_k is the current flowing through the branch.

TELLEGEN THEOREM

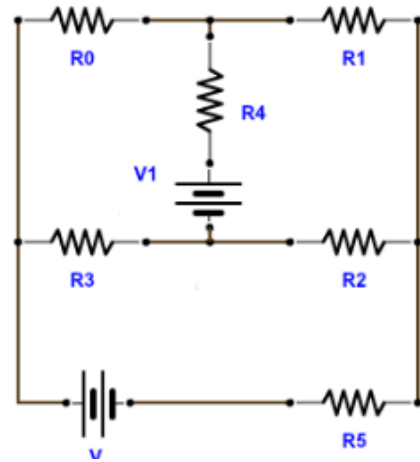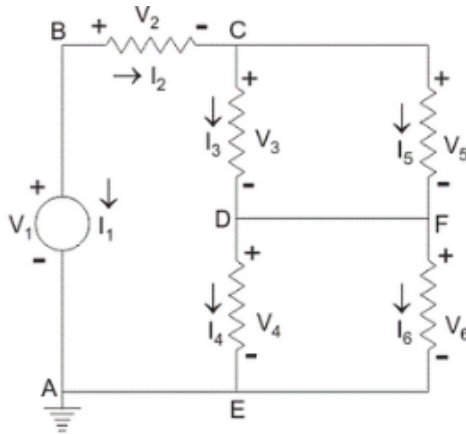

This theorem can easily be explained by the following example.

Thus, it has been observed that the sum of power delivered to a closed network is zero. This proves the Tellegen's theorem and also proves the conservation of power in any electrical network.

It is also evident that the sum of power delivered to the network by an independent source is equal to the sum of power absorbed by all passive elements of the network.


APPLICATION OF TELLEGEN'S THEOREM

The various applications of the **Tellegen's theorem** are as follows:

- It is used in the digital signal processing system for designing filters.
- In the area of the biological and chemical process.
- In topology and structure of reaction network analysis.
- The theorem is used in chemical plants and oil industries to determine the stability of any complex systems.

It is also used in complex operating systems for regulating stability. It is mostly used in the chemical and biological system and for finding the dynamic behaviour of the physical network

PROCEDURE

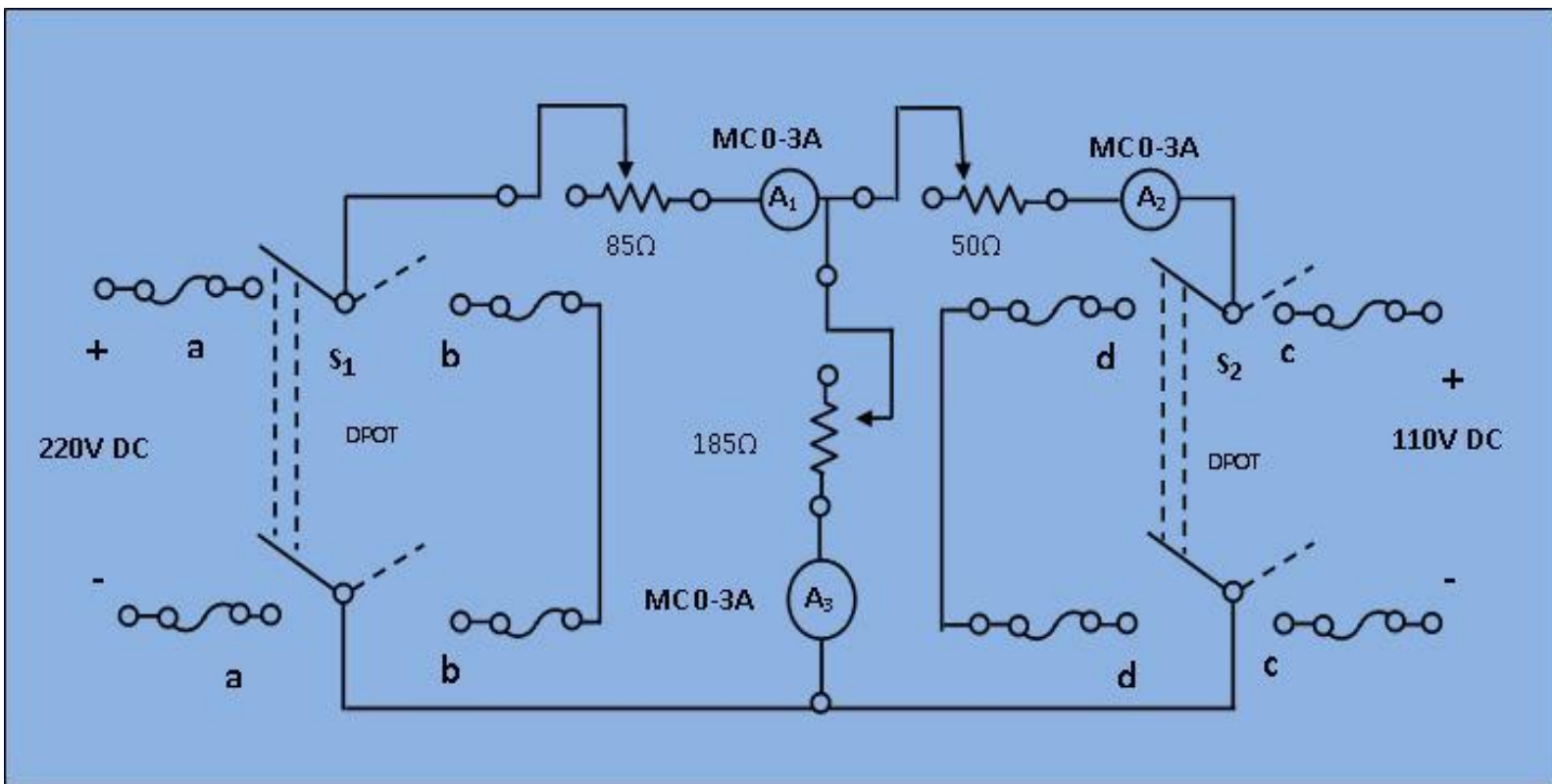

CIRCUIT DIAGRAM OF EXPERIMENTAL SET-UP FOR VERIFICATION OF
TELLEGEN'S THEOREM

Connect the circuit as shown in the circuit diagram above, keeping the switches open and resistance at their maximum positions.

1. **Case 1:** In presence of both the sources

Select switch of S_1 to Power and S_2 to Power and switch on the supply to get the ammeter readings. Observe the power supplied in +ve and power dissipated in -ve by the elements and voltage source for this condition.

2. **Case-2:** In presence of V_1 only

Select switch of S_1 to Power and S_2 to short and switch on the supply. Read the corresponding power values as done in the above case.

3. **Case-3:** In presence of V_2 only


Select switch of S_1 to Short and S_2 to switch on the supply. Read the corresponding power values.

Calculate the power consumed or delivered by each element for each case and check if
POWER ABSORBED = POWER DELIVERED.

THIS PROVES THE TELLEGEN'S THEOREM.

OBSERVATIONS

THE READINGS ARE TAKEN FROM THE VLABS

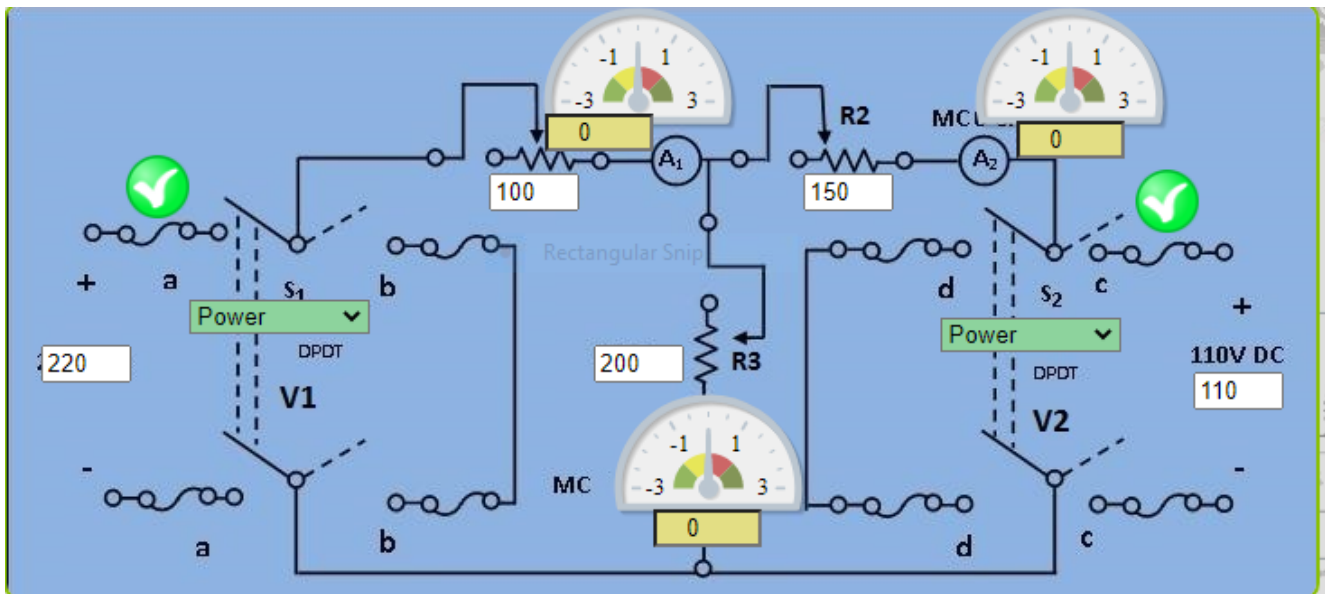

Case 1

Case 2

Case 3

Determination of branch currents in presence of both the sources:

Select both the switches, S₁ and S₂ to power.

And then click on Simulate. All powers are in Watt.

Simulate

$P_1(\text{by } R_1) + P_2(\text{by } R_2) + P_3(\text{by } R_3) + P_{v1}(\text{by } V_1) + P_{v2}(\text{by } V_2) = \text{Result of summation}$

0

0


0

0

0

0

READING 1

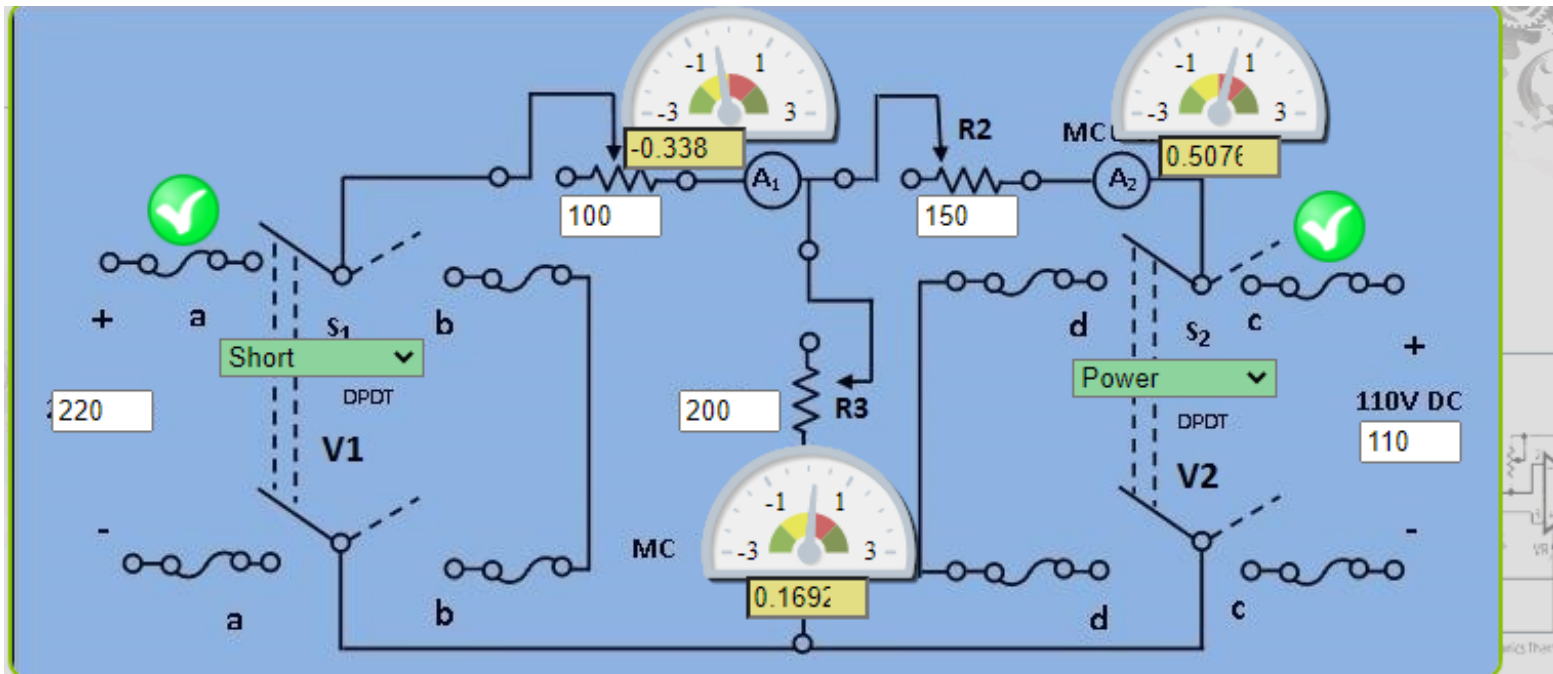

Case 1

Case 2

Case 3

Determination of branch currents in presence of V_2 source only:

Select both the switch S_1 to short and S_2 to power.

And then click on Simulate. All powers are in Watt.

$P_1(\text{by } R_1) + P_2(\text{by } R_2) + P_3(\text{by } R_3) + P_{V2}(\text{by } V_2) = \text{Result of summation}$

-11.455621

-38.662721

-5.7278106


55.8461536

0

Simulate

Fill data to the table

READING 2

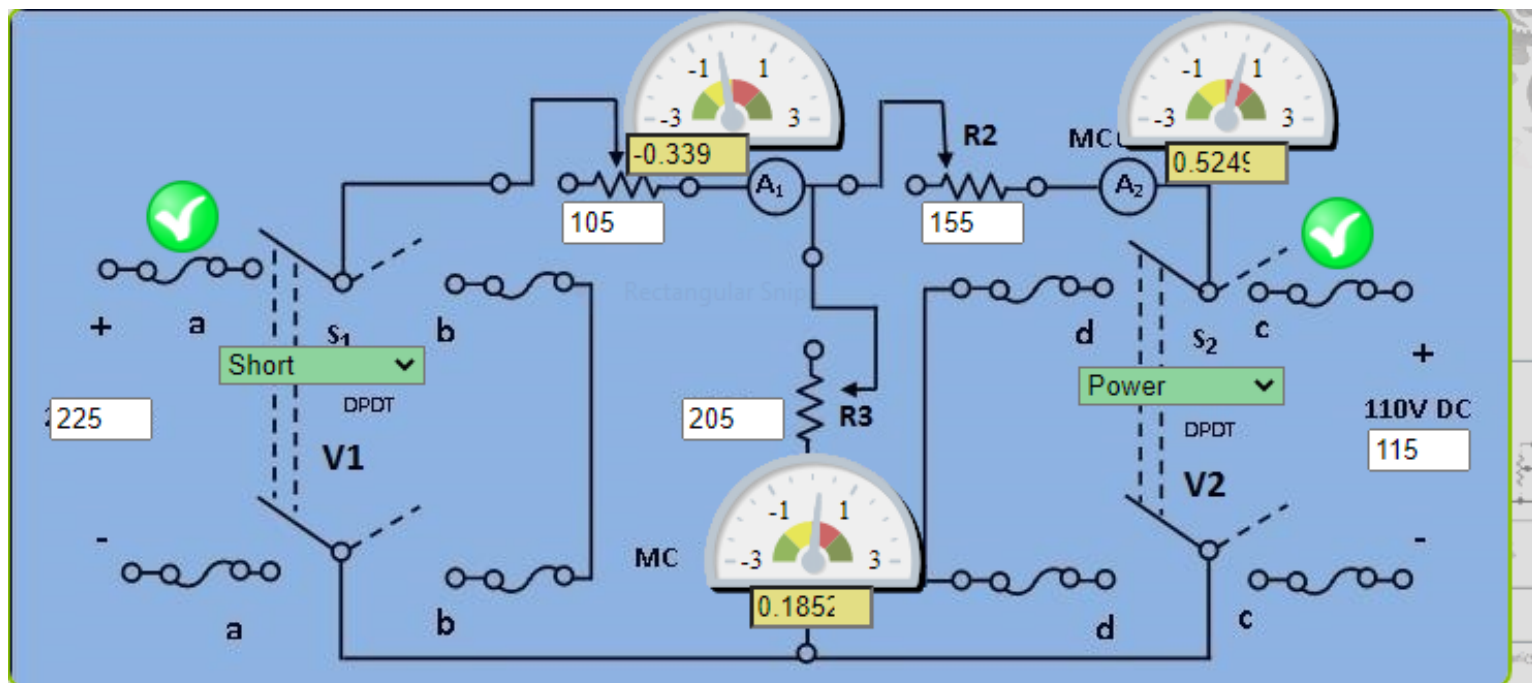

Case 1

Case 2

Case 3

Determination of branch currents in presence of V_2 source only:

Select both the switch S_1 to short and S_2 to power.

And then click on Simulate. All powers are in Watt.

$P1(\text{by } R1) + P2(\text{by } R2) + P3(\text{by } R3) + P_{V2}(\text{by } V2) = \text{Result of summation}$

-12.114268

-42.712211

-7.0368594


60.3681710

0

Simulate

Fill data to the table

READING 3

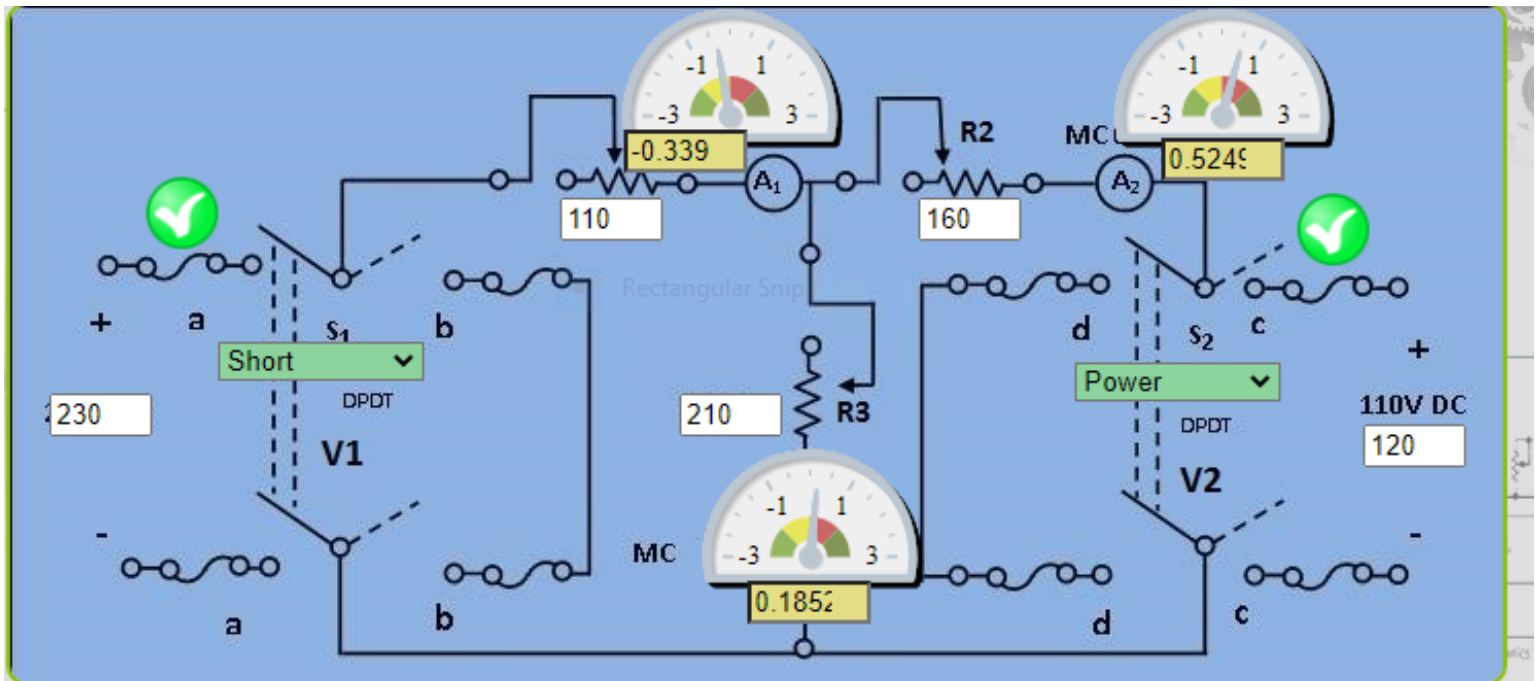

Case 1

Case 2

Case 3

Determination of branch currents in presence of V_2 source only:

Select both the switch S_1 to short and S_2 to power.

And then click on Simulate. All powers are in Watt.

$P_1(\text{by } R_1) + P_2(\text{by } R_2) + P_3(\text{by } R_3) + P_{V2}(\text{by } V_2) = \text{Result of summation}$

-12.691138

-44.090024

-7.2084901


62.9928741

0

Simulate

Fill data to the table

READING 4

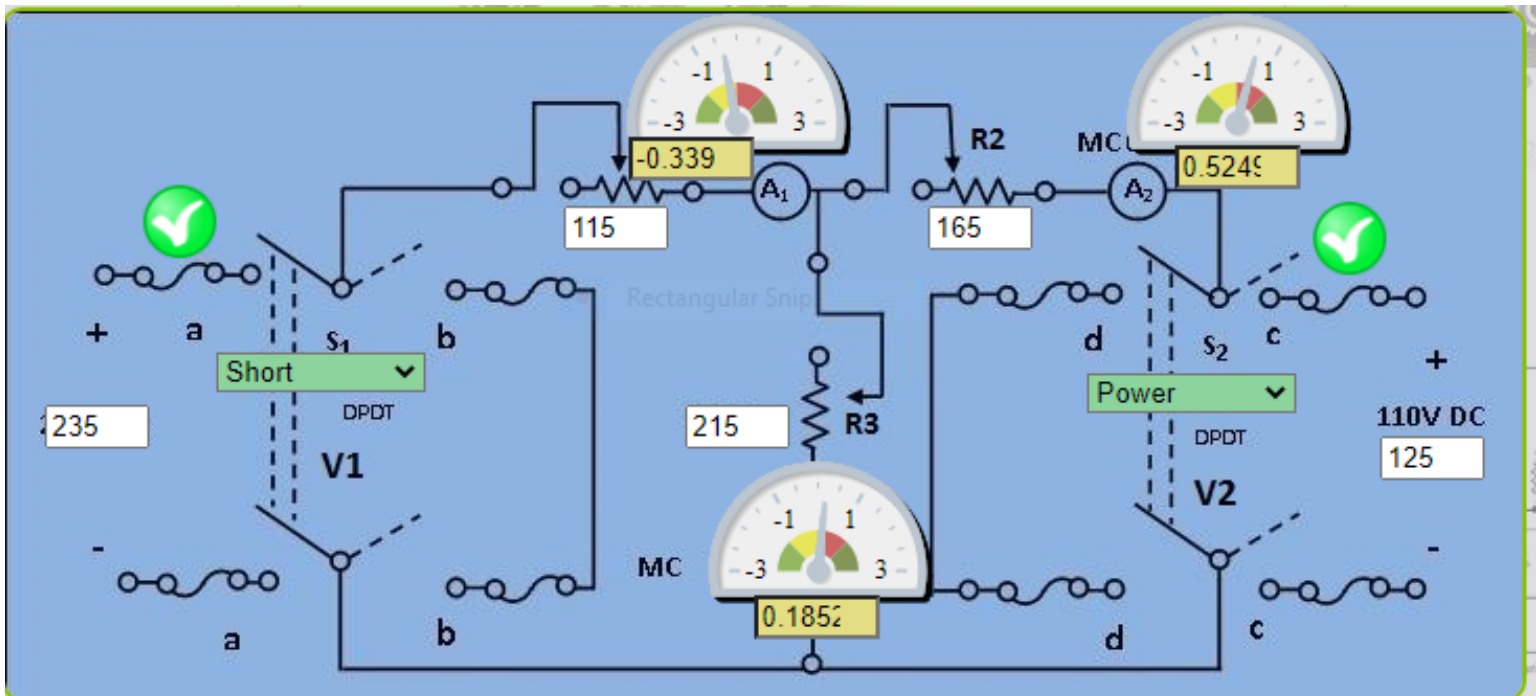

Case 1

Case 2

Case 3

Determination of branch currents in presence of V_2 source only:

Select both the switch S_1 to short and S_2 to power.

And then click on Simulate. All powers are in Watt.

$P_1(\text{by } R_1) + P_2(\text{by } R_2) + P_3(\text{by } R_3) + P_{V2}(\text{by } V_2) = \text{Result of summation}$

-13.268007

-45.467837

-7.3801208


65.6175771

0

Simulate

Fill data to the table

READING 5

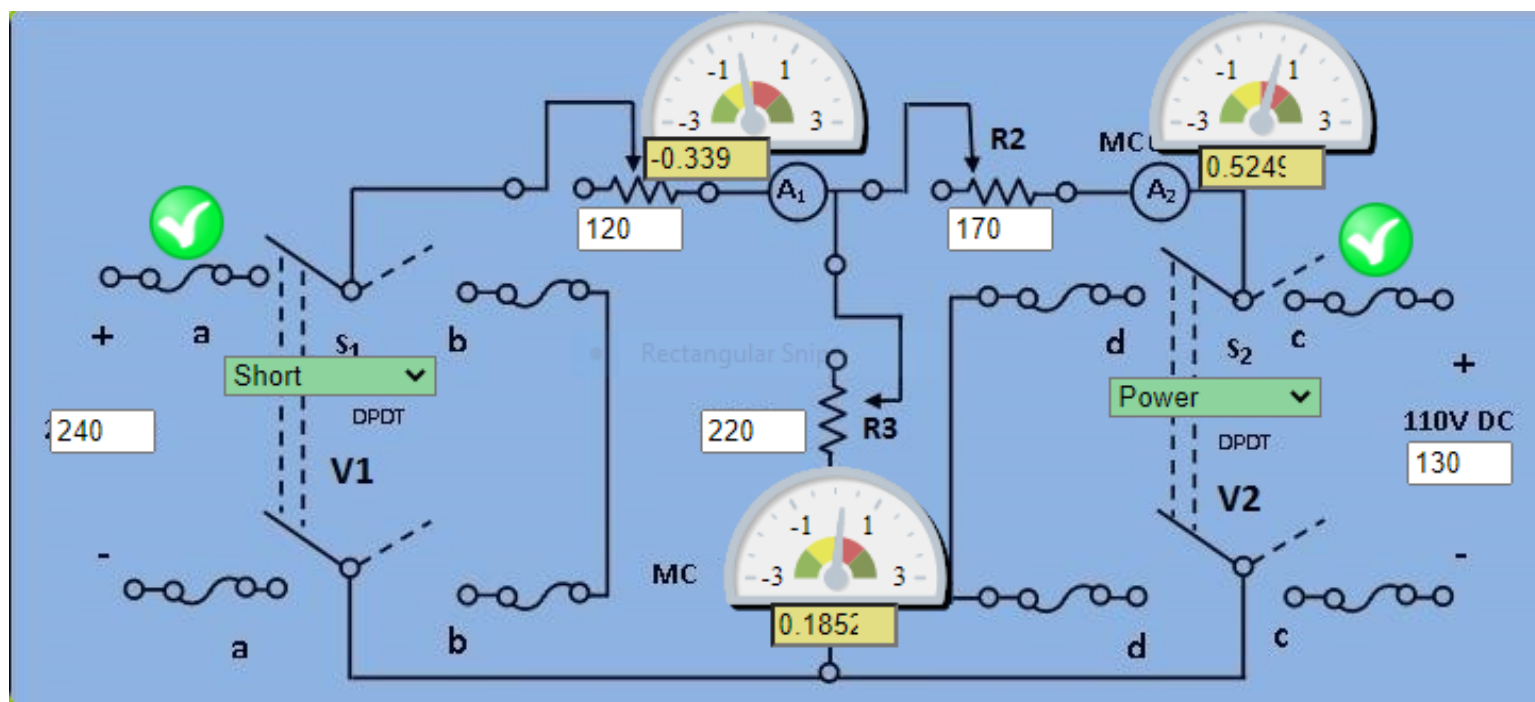

Case 1

Case 2

Case 3

Determination of branch currents in presence of V_2 source only:

Select both the switch S_1 to short and S_2 to power.

And then click on Simulate. All powers are in Watt.

$P1(\text{by } R1) + P2(\text{by } R2) + P3(\text{by } R3) + P_{v2}(\text{by } V2) = \text{Result of summation}$

-13.844877

-46.845650

-7.5517515

68.2422802

0

Simulate

Fill data to the table

OBSERVATION TABLE

Observation Table:

Sl no.	In presence of both V_1 and V_2 All values are in Watt					In presence of V_1 only All values are in Watt				In presence of V_2 only All values are in Watt			
	P_1 (by R_1)	P_2 (by R_2)	P_3 (by R_3)	P_{V_1} (by V_1)	P_{V_2} (by V_2)	P_1 (by R_1)	P_2 (by R_2)	P_3 (by R_3)	P_{V_1} (by V_1)	P_1 (by R_1)	P_2 (by R_2)	P_3 (by R_3)	P_{V_2} (by V_2)
1	-71.5	-4.29	-91.6	186.1	-18.6	-140.	-68.7	-51.5	260.6	-11.4	-38.6	-5.72	55.84
2	-71.5	-3.51	-93.3	185.7	-17.3	-142.	-68.1	-51.5	261.9	-12.0	-40.6	-6.17	58.92
3	-71.4	-2.84	-95.1	185.4	-15.9	-144.	-67.6	-51.5	263.4	-12.6	-42.7	-6.62	62.01
4	-71.4	-2.26	-96.8	185.2	-14.6	-146.	-67.1	-51.5	265.0	-13.2	-44.7	-7.08	65.12
5	-71.5	-1.77	-98.7	185.2	-13.2	-148.	-66.8	-51.6	266.7	-13.8	-46.8	-7.55	68.24

RESULT/CONCLUSION :-

THE ABOVE READINGS OF THE **OBSERVATION TABLE** AS THE SUMMATION OF ALL **POWER** VALUES EQUALS TO **ZERO** WHICH VERIFIES THE

TELLENGEN'S THEOREM

HENCE , TELLENGEN THEOREM HAS BEEN VERIFIED

