

# ELECTRICAL ASSIGNMENT

## 4

Ques 1:- Calculate the active and reactive current components in each phase of a star connected 10,000 V, 3 phase alternator supplying 5000 kW at a power factor of 0.8. If the total current remains same when the load power factor is raised to 0.9, find the new output.

Sol<sup>n</sup>:- Power supplied ( $P$ ) =  $\sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi = 5000 \text{ kW}$

$$\text{Line current } (I_L) = \frac{5000}{\sqrt{3} \cdot V_L \cdot \cos \phi} = \frac{5000}{\sqrt{3} \times 10,000 \times 0.8} \Rightarrow I_L = I_p = 360.844$$

$$\text{Active component of current in each phase} = I_p \cos \phi = 288.7 \text{ A}$$

$$\text{Reactive component of current in each phase} = I_p \sin \phi = 216.5 \text{ A}$$

New output when p.f. is raised to 0.9 keeping total current remains same.

$$P' = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi = \sqrt{3} \times 10,000 \times 360.8 \times 0.9$$

$$P' = 5625 \text{ kW}$$

Ques 2:- A 3-phase star connection alternator feeds a 2000 hp delta-connected induction motor having a p.f. of 0.85 & efficiency of 0.93. Calculate total current and active & reactive current components in (a) each alternator phase  
The line voltage is 2200 V. (b) each motor phase

$$\text{Original power} = \frac{2000 \times 746}{0.93}$$

$$P = 1604.301 \text{ kW}$$

$$P = 3 V_p I_p \cos \phi$$

$$I_p = \frac{P}{3 V_p \cos \phi}$$

$$(a) I_p = \frac{P \sqrt{3}}{3 V_L \cos \phi} = 496 \text{ A}$$


$$\text{Active comp. of current} = 421 \text{ A}$$

$$\text{Reactive comp of current} = 262 \text{ A}$$

$$(b) I_p = \frac{P}{3 V_L \cos \phi} = 286 \text{ A}$$

$$\text{Active comp of current} = 243 \text{ A}$$

$$\text{Reactive comp of current} = 151 \text{ A}$$

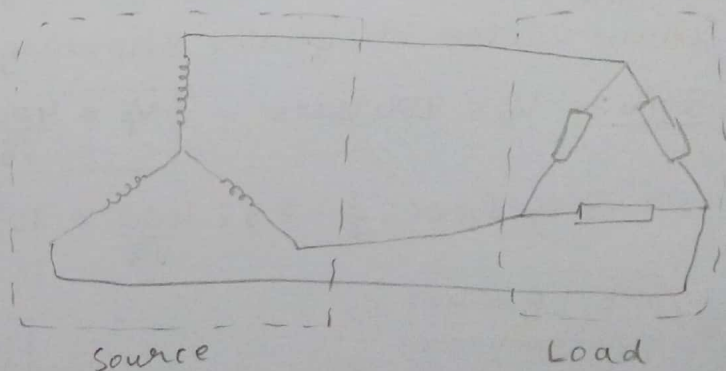



Ques 3:- A balanced star connected load  $(8+j6)\Omega$  per phase is connected to a 3 phase, 230V supply. Find the line current, power factor, power, reactive power (VA) & total volt ampere.

$$\vec{Z} = 8 + j6 \quad |\vec{Z}| = 10\Omega \quad V_L = 230 \quad V_P = \frac{230}{\sqrt{3}} \quad I_P = \frac{V_P}{Z} = \frac{23}{\sqrt{3}} = 13.3$$

$$P.f = \cos \phi = \frac{8}{10} = 0.8$$

$$P = 3 V_P I_P \cos \phi = 3 \times \frac{230}{\sqrt{3}} \times \frac{23}{\sqrt{3}} \times 0.8$$

$$P = 4232 \text{ W}$$

$$\text{Reactive volt ampere} = 3 V_P I_P \sin \phi = 3174 \text{ VA}$$

$$\text{Total volt ampere} = 3 V_P I_P = 5290 \text{ VA}$$

Ques 4:- A balanced 3- $\phi$  Y connected load of 150 kW takes a leading current of 100A with a line voltage 1100V, 50 Hz. Find the circuit constants of the load per phase.

$$V_L = 1100 \text{ Volts} \quad V_P = \frac{1100}{\sqrt{3}} \quad \omega = 50 \text{ Hz} \quad \text{Power in each phase} = 50 \text{ kW}$$

$$\text{So, } 50 \times 10^3 = \frac{1100}{\sqrt{3}} \times 100 \times \cos \phi$$

$$\cos \phi = \frac{5\sqrt{3}}{11}$$

$$Z = \frac{V_P}{I_P} = \frac{1100}{\sqrt{3} \times 100} = \frac{11}{\sqrt{3}}$$

$$R = Z \cos \phi = \frac{11}{\sqrt{3}} \times \frac{5\sqrt{3}}{11}$$

$$R = 5\Omega$$

$$X_C = Z \sin \phi = \frac{11}{\sqrt{3}} \sqrt{1 - \frac{75}{121}} = \frac{11}{11} \frac{\sqrt{46}}{\sqrt{3}} = \sqrt{\frac{46}{3}}$$

$$C = \frac{\sqrt{3}}{100\pi \sqrt{46}}$$

$$C = 810 \mu\text{F}$$

Ques 5: A balanced Y connected load is supplied from a sym. 3  $\phi$ , 400V system. The current in each phase is 30A and lags  $30^\circ$  behind the phase voltage. Find (a) the phase voltage.

(b) the total power.

Draw vector diagram showing the current and voltages.

Soln:-  $V_L = 400 \text{ Volts}$

$$V_P = \frac{400}{\sqrt{3}} = 231 \text{ Volts}$$

$$P = 3 V_P I_P \cos \phi = 3 \times \frac{400}{\sqrt{3}} \times 30 \times \cos 30^\circ = 3 \times \frac{400}{\sqrt{3}} \times 30 \times \frac{\sqrt{3}}{2}$$

$$P = 18 \text{ kW}$$



Ques 6:- Three equal star connected inductors take 8 kW at power factor 0.8 when connected to 460V, 3 phase, 3 wire supply. Find the line currents if one inductor is short circuited.


Sol<sup>n</sup>:-  $P = \sqrt{3} V_L I_L \cos \phi$

$$I_L = \frac{P}{\sqrt{3} V_L \cos \phi} = \frac{8 \times 10^3}{\sqrt{3} \times 460 \times 0.8}$$

$$I_L = 12.55 \text{ A}$$

$$\text{Phase Impedance} = \frac{V_p}{I_p} = \frac{460}{\sqrt{3} \times 12.55}$$

$$= 21.16 \Omega$$

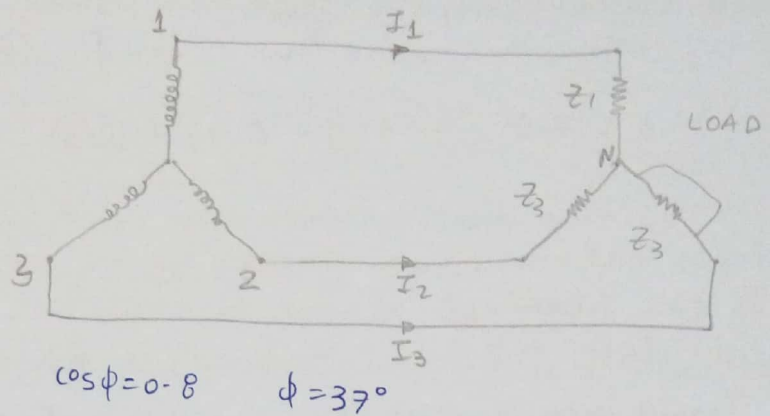

Since  $Z_3$  is short circuit, then 3 & N are at same potential.

The three line voltage as phasors will be

$$V_{12} = 460 \angle 0^\circ \quad V_{23} = 460 \angle -120^\circ \quad V_{31} = 460 \angle 120^\circ$$

Since 3 & N are at same potential

$$\vec{I}_1 = \frac{\vec{V}_{13}}{Z} = \frac{-460 \angle 120^\circ}{21.16 \angle 37^\circ} \quad \vec{I}_1 = -21.7 \angle 83^\circ \text{ A} = -2.64 - j(21.5) \text{ A}$$

$$\vec{I}_2 = \frac{\vec{V}_{23}}{Z} = \frac{460 \angle -120^\circ}{21.16 \angle 37^\circ} \quad 21.7 \angle -157^\circ = \vec{I}_2 = -19.97 - j(8.48) \text{ A}$$

$$\vec{I}_3 = -(\vec{I}_1 + \vec{I}_2) \quad (\text{As at N } \vec{I}_1 + \vec{I}_2 + \vec{I}_3 = 0)$$

$$\vec{I}_3 = (19.97 + 2.64) + j(8.48 + 21.5) \text{ A}$$

$$I_3 = 22.61 + j(29.98) = 37.6 \angle 53^\circ \text{ A}$$

Ques 7:-  $\vec{V}_{RB} = \vec{V}_R - \vec{V}_B$  &  $\vec{V}_{YB} = \vec{V}_Y - \vec{V}_B$

$$\angle \text{b/w } \vec{V}_{RB} \text{ \& } \vec{I}_R = 30 - \phi$$

$$\angle \text{b/w } \vec{V}_{YB} \text{ \& } \vec{I}_Y = 30 + \phi$$

$$W_1 = V_{RB} I_R \cos(30 - \phi) = \sqrt{3} V_p I_p \cos(30 - \phi)$$

$$W_2 = V_{YB} I_Y \cos(30 + \phi) = \sqrt{3} V_p I_p \cos(30 + \phi)$$

$$W_1 + W_2 = \sqrt{3} V_p I_p [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= \sqrt{3} V_p I_p [2 \cos 30 \cos \phi]$$

$$= 3 V_p I_p \cos \phi$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Also } \frac{W_1}{W_2} = \frac{\cos(30 - \phi)}{\cos(30 + \phi)}$$

$$\Rightarrow \frac{W_1 - W_2}{W_1 + W_2} = \frac{\cos(30 - \phi) - \cos(30 + \phi)}{\cos(30 - \phi) + \cos(30 + \phi)}$$

$$\frac{W_1 - W_2}{W_1 + W_2} = \frac{2 \sin 30 \sin \phi}{2 \cos 30 \cos \phi} = \tan 30^\circ \tan \phi$$


$$\tan \phi = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2}$$

$$\tan \phi = \sqrt{3} \left( \frac{1200 - 300}{1200 + 300} \right) = \sqrt{3} \times \frac{900}{1500}$$

$$= 1.04$$

$$\phi = 46.102^\circ$$

$$\cos \phi = 0.6934 \text{ lag}$$

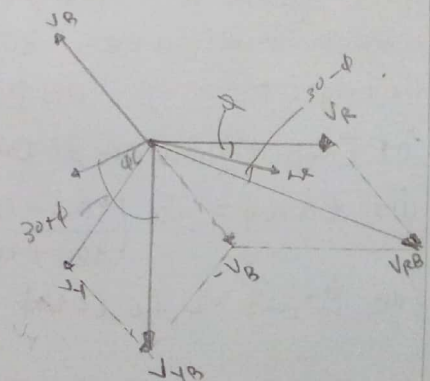



Ques 8:- A 3- $\phi$  balanced load power was measured by two wattmeter. If readings of the two wattmeters so connected are 5 and 0.5 kW, the latter reading being obtained after reversal of current coil connections, calculate the power factor of the load.

$$W_1 = 5 \text{ kW} \quad W_2 = -0.5 \text{ kW} \quad \tan \phi = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2} = \sqrt{3} \left( \frac{5.5}{4.5} \right) = \sqrt{3} \times \frac{11}{9}$$

$$\phi = 64.715^\circ \quad \cos \phi = 0.427 \text{ (lag)}$$

Ques 9:- Two wattmeters are used for measuring the power input and the power factor of an overexcited synchronous motor. If the readings of the meters are -2 & +7 kW respectively, calculate the input and power factor of motor.

$$\text{Input power} = W_1 + W_2 = -2 + 7 = 5 \text{ kW}$$

$$\tan \phi = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2} = \sqrt{3} \left( \frac{-2 - 7}{5} \right) = \frac{-9\sqrt{3}}{5} \quad \phi = 72.216$$

$$\text{P.f} = \cos \phi = 0.3054 \text{ (lead)}$$

Ques 10:- A 3-phase delta connected balanced load consist of a resistance of  $10 \Omega$  in series with an inductive reactance of  $17.32 \Omega$ . If the circuit is connected to a 440V, 50 Hz supply and the total power consumed is 14,520 W, what is the reading read by each wattmeter if the power is measured by 2 wattmeter method?

$$R = 10 \Omega \quad X = 17.32 = 10\sqrt{3} \quad Z = 20 \quad \cos \phi = \frac{1}{2} \quad \phi = 60^\circ$$

$$\tan \phi = \sqrt{3} \quad \sqrt{3} = \tan \phi = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2} \quad W_1 - W_2 = W_1 + W_2$$

$$2W_2 = 0 \quad W_2 = 0$$

$$W_1 = 14,520 \text{ W}$$

$$W_2 = 0$$

Ques 11:- The power input to a 2000V, 50 Hz, 3- $\phi$  motor running on full load at efficiency of 90% is measured by two wattmeter which indicates 300 kW & 100 kW respectively. calculate  
(i) input ; (ii) power factor ; (iii) line current (iv) hp output.

$$(i) \text{ Input power} = W_1 + W_2 = 400 \text{ kW}$$

$$(ii) \tan \phi = \sqrt{3} \left( \frac{300 - 100}{300 + 100} \right) = \frac{\sqrt{3}}{2} \quad \phi = 40.893 \quad \cos \phi = 0.756$$

$$(iii) P = \sqrt{3} V_L I_L \cos \phi \quad I_L = \frac{400 \times 10^3}{\sqrt{3} \times 2 \times 10^3 \times 0.756} \quad I_L = 152 \text{ A}$$

$$(iv) \text{ Output power} = 400 \times 0.9 = 360 \text{ kW} = \frac{360 \times 10^3}{735} = 490 \text{ metric hp}$$

Ques 12:- A 3- $\phi$  motor draws a line current of 50 A from 220 V source while starting. The p.f. is 0.4. Find the reading of the two wattmeters connected to measure power.

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 220 \times 50 \times 0.4 = 7.62 \text{ kW}$$

Let the readings of two wattmeters be  $x$  &  $y$ .

$$x + y = 7.62 \quad \text{--- (i)} \quad \cos \phi = 0.4 \quad \phi = 66.422^\circ \quad \tan \phi = 89.1374$$

$$\tan \phi = \sqrt{3} \left( \frac{x - y}{x + y} \right) \quad x - y = 10.08 \quad \text{--- (ii)}$$

On solving (i) & (ii), we get  $x = 8.85$  &  $y = -1.23$

Reading of wattmeter are 8.85 kW & -1.23 kW